CENG 215 Circuits and Electronics

LAB #1 Feuille


Place: PC Lab

Aim

To build resistive networks on a circuit simulator, to measure the voltages and currents and to compare the measurements with the theoretical analysis results.


Work to be done:

1. Build the following circuit.

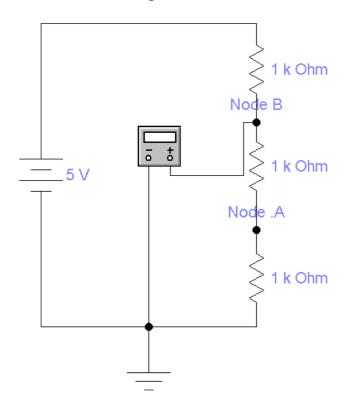

- 2. Measure the voltage of the voltage source, measure the resistance values of three resistors. Using the measured values, analyze the circuit (Calculate the current and voltages of Node A and Node B).
- 3. Measure the voltages of Node A and Node B.

4. Measure the current as follows:

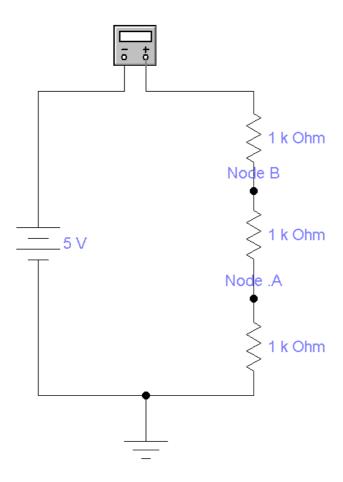

5. Compare the results of the theoretical analysis and your measurements. Are there differences? Comment on this.

Final Remarks

Repeat the same work on PySpice.