CENG 215 Circuits and Electronics

LAB #4 Feuille

Place: PC Lab

Aim


To build and analyze various resistive networks in PySpice and to compare the analysis results with the theoretical analysis results.

Materials/Devices:

PySpice

Work to be done:

 The following circuit is a first order R-C circuit. Assume that the capacitor is initially discharged and 10V voltage source is applied at time zero.



- 1. Simulate the circuit and plot the capacitor voltage $V_c(t)$.
 - a. Try these voltage sources and discuss the results:

```
source = circuit.VoltageSource('input', 'in', circuit.gnd, 10@u_V)
source = circuit.PieceWiseLinearVoltageSource('input', 'in', circuit.gnd, values=[(0,0),(0,10@u_V)])
source = circuit.PulseVoltageSource('input', 'in', circuit.gnd, initial_value=0@u_V, pulsed_value=10@u_V, pulse_width=100@u_ms, period=200@u_ms)
```

- b. What is V_c at $t=20\mu s$? Find it both theoretically and by simulation.
- c. In transient simulation, change the "step_time" parameter and observe its effect.

Final Remarks