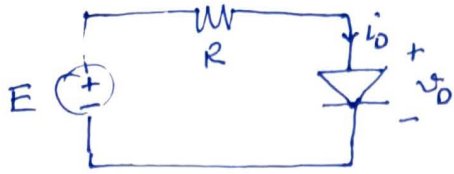


NONLINEAR CIRCUITS

③

Solve analytically non-linear circuit with diode:



$$\frac{v_D - E}{R} + i_D = 0$$

$$i_D = I_S (e^{v_D/V_{TH}} - 1)$$

$$\Rightarrow \frac{v_D - E}{R} + I_S (e^{v_D/V_{TH}} - 1) = 0$$


not easy to solve!

numerical solution seems easier.


Graphical analysis:

$E = 3V$, $R = 500\Omega$, find i_D , v_D ?


$$i_D = \frac{E - v_D}{R}$$

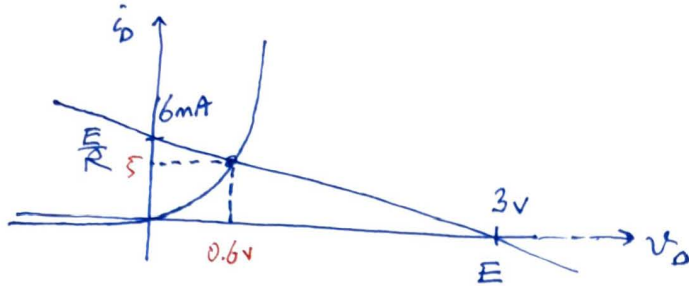

Piecewise Linear Analysis

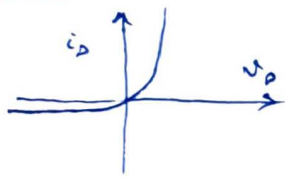

Assumption:


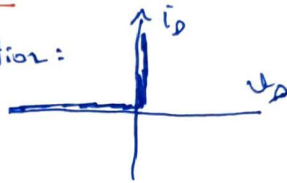


Diode ON (short circuit):



$v_D = 0$ for all $i_D > 0$

Diode OFF (open circuit):

$i_D = 0$ for all $v_D < 0$.

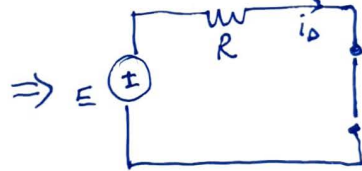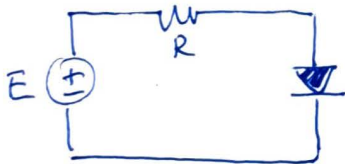


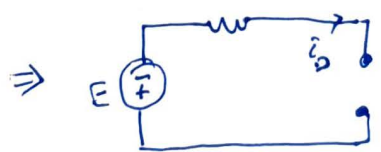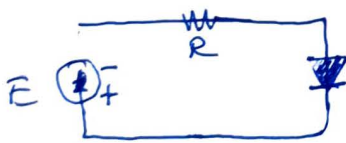Short circuit ($v_D = 0$, $i_D = \frac{E}{R}$)




Open circuit ($v_D = E$, $i_D = 0$)

A hypothetical device:


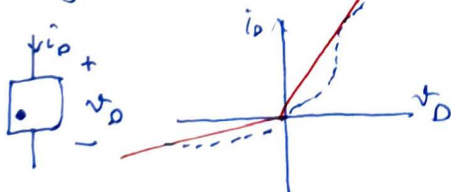


for $i_D < 0$, slope = $\frac{1}{R_2}$ ($R_2 = 10k\Omega$)

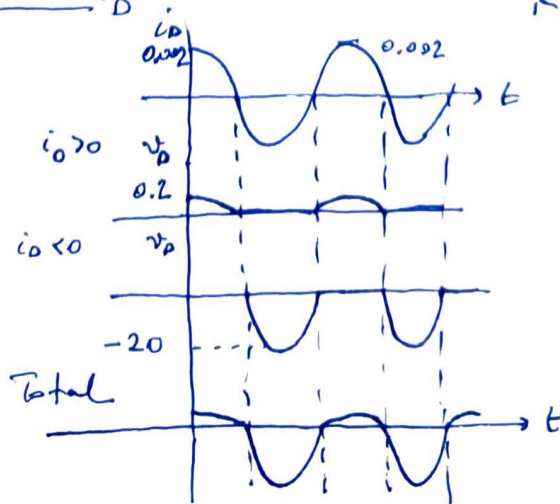for $i_D > 0$, slope = $\frac{1}{R_1}$ ($R_1 = 100\Omega$)



Incremental Analysis:

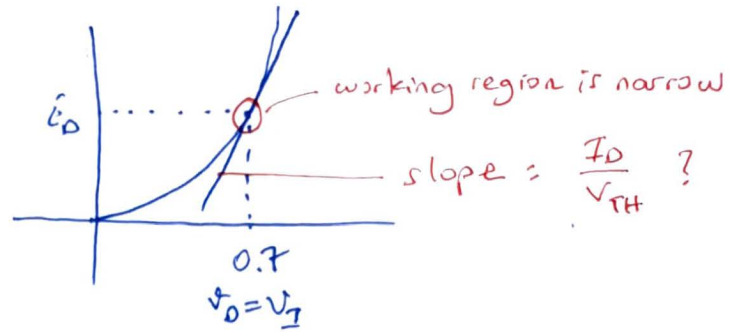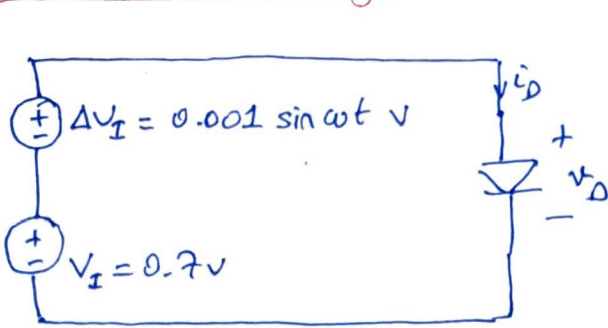

Taylor at V_D :
exp.

$$i_D = I_s (e^{(0.7 + 0.001 \sin \omega t) / V_{TH}} - 1)$$

$$i_D = f(v_D) = f(V_D) + \left. \frac{df}{dv_D} \right|_{V_D} (v_D - V_D) + \frac{1}{2!} \left. \frac{d^2f}{dv_D^2} \right|_{V_D} (v_D - V_D)^2 + \dots$$

We wish to expand diode equation $i_D = I_s (e^{(v_D + \Delta v_D) / V_{TH}} - 1)$ about the point V_D, I_D . when we apply $v_D = V_D + \Delta v_D$, the current will be $i_D = I_D + \Delta i_D$.

Taylor expansion:

$$i_D = I_s (e^{v_D / V_{TH}} - 1) + \frac{1}{V_{TH}} (I_s e^{v_D / V_{TH}}) \Delta v_D + \frac{1}{2} \left(\frac{1}{V_{TH}} \right)^2 I_s e^{v_D / V_{TH}} (\Delta v_D)^2 + \dots$$

Simplifying: $i_D = I_s (e^{v_D / V_{TH}} - 1) + (I_s e^{v_D / V_{TH}}) \left[\frac{1}{V_{TH}} \Delta v_D + \frac{1}{2} \left(\frac{1}{V_{TH}} \right)^2 (\Delta v_D)^2 + \dots \right]$

Δv_D is very small compared to V_{TH} (0.025 V), so we can ignore higher order terms: 0.001

$$i_D = \underbrace{I_s (e^{v_D / V_{TH}} - 1)}_{I_D} + \underbrace{I_s e^{v_D / V_{TH}}}_{\Delta i_D} \cdot \frac{1}{V_{TH}} \cdot \Delta v_D$$

This is $I_D + \Delta i_D \Rightarrow$

$$\Delta i_D = \underbrace{(I_s e^{v_D / V_{TH}})}_{I_D} \cdot \frac{1}{V_{TH}} \cdot \Delta v_D \quad (\text{Linear equation})$$

$$\Delta i_D = I_D \cdot \frac{1}{V_{TH}} \cdot \Delta v_D \Rightarrow \text{slope of the line} = \frac{I_D}{V_{TH}}$$

For more accurate calculation we can take higher terms of Taylor.

$$v_D = V_D + \Delta v_D = 0.7 \text{ V} + 0.001 \text{ V} \cdot \sin \omega t$$

so Δv_D is small enough: $i_D = I_D + \Delta i_D$ $I_D = I_s (e^{0.7 / V_{TH}} - 1)$

$$\Delta i_D = \left. \frac{df}{dv_D} \right|_{V_D} \Delta v_D = I_s e^{0.7 / V_{TH}} \cdot \frac{1}{V_{TH}} \cdot 0.001 \sin \omega t$$

$$I_D = 1.45 \text{ A}, \quad \Delta i_D = 0.058 \text{ A} \cdot \sin \omega t$$