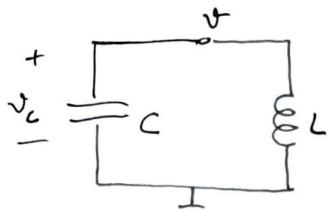


Undriven L-C circuit:



Undriven response is also known as Zero Input Response (ZIR) of circuit

$$C \frac{dv(t)}{dt} + \frac{1}{L} \int_{-\infty}^t v(t) dt = 0 \Rightarrow \frac{d^2 v(t)}{dt^2} + \frac{1}{LC} v(t) = 0$$

we set Ae^{st} or using Laplace

$$As^2 e^{st} + A \frac{1}{LC} e^{st} = 0 \Rightarrow A \underbrace{\left(s^2 + \frac{1}{LC}\right)}_0 e^{st} = 0$$

$$s_1 = +j\omega_0 \quad \text{where } \omega_0 = \frac{1}{\sqrt{LC}}$$

$$s_2 = -j\omega_0$$

Since $j = \sqrt{-1}$. The solution for v is linear combination of $e^{s_1 t}$ and $e^{s_2 t}$.

$$\text{so } v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} = A_1 e^{j\omega_0 t} + A_2 e^{-j\omega_0 t}$$

$e^{jx} = \cos x + j \sin x$

Therefore we can write: $v(t) = K_1 \cos \omega_0 t + K_2 \sin \omega_0 t$

we calculate K_1 and K_2 using $v(0)$, $\frac{dv}{dt}(0)$ initial values.

$$e^{j\omega_0 t} + e^{-j\omega_0 t} = 2 \cos \omega_0 t$$

$$e^{j\omega_0 t} - e^{-j\omega_0 t} = 2j \sin \omega_0 t$$

$$v(0) = K_1 \cos 0 + K_2 \sin 0 = K_1 \quad \frac{dv}{dt}(0) = \omega_0 K_2 \Rightarrow K_2 = \frac{1}{\omega_0} \frac{dv}{dt}(0)$$

$$\text{so } v(t) = v(0) \cos \omega_0 t + \frac{1}{\omega_0} \frac{dv}{dt}(0) \sin(\omega_0 t)$$


Or using Laplace Transform:

$$\frac{d^2 v(t)}{dt^2} + \frac{1}{LC} v(t) = 0 \Rightarrow s^2 V(s) - s v(0) - \dot{v}(0) + \frac{1}{LC} V(s) = 0$$

$$V(s) = \frac{s v(0) + \dot{v}(0)}{s^2 + \frac{1}{LC}} = \frac{s v(0) + \dot{v}(0)}{s^2 + \omega_0^2} = \underbrace{\frac{A s}{s^2 + \omega_0^2}}_{\text{cosine}} + \underbrace{\frac{B \omega_0}{s^2 + \omega_0^2}}_{\text{sine}}$$

$$\Rightarrow s v(0) = A s \quad B \omega_0 = \dot{v}(0) \Rightarrow v(t) = v(0) \cos \omega_0 t + \frac{1}{\omega_0} \dot{v}(0) \sin \omega_0 t$$

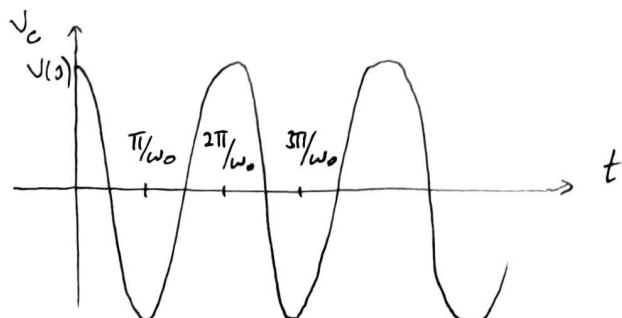
$$A = v(0) \quad B = \frac{1}{\omega_0} \dot{v}(0)$$



SECOND-ORDER CIRCUITS/SYSTEMS

(2)

Undriven series RLC:

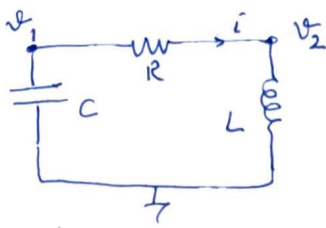

$$\text{KCL @ Node 1: } C \frac{dv_1}{dt} + \frac{v_1 - v_2}{R} = 0$$

$$\text{KCL @ Node 2: } \frac{v_2 - v_1}{R} + \frac{1}{L} \int_{-\infty}^t v_2 dt = 0$$

$$\text{or } Ri + L \frac{di}{dt} + \frac{1}{C} \int i dt = 0$$

$$\Rightarrow \ddot{i} + \frac{R}{L} \dot{i} + \frac{1}{LC} i = 0 \quad \frac{d^2}{dt^2} i(t) + \frac{R}{L} \frac{d}{dt} i(t) + \frac{1}{LC} i(t) = 0$$

$$i = A e^{st} \text{ is the solution. } \Rightarrow \underbrace{A(s^2 + \frac{R}{L}s + \frac{1}{LC})}_{\text{characteristic equation}} = 0$$

we use this general form for characteristic equation of 2nd order circuits:

$$s^2 + 2\alpha s + \omega_0^2 = 0 \quad \text{where } \alpha \equiv \frac{R}{2L}, \quad \omega_0 \equiv \frac{1}{\sqrt{LC}}$$

$$\text{so the roots: } s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$$

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

Decaying and oscillatory shape!

Therefore the solution is linear combination of $e^{s_1 t}$ and $e^{s_2 t}$:

$$i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

we have three cases:


$$\begin{aligned} \alpha < \omega_0 &\Rightarrow \text{under-damped dynamics} \\ \alpha = \omega_0 &\Rightarrow \text{critically-damped dynamics} \\ \alpha > \omega_0 &\Rightarrow \text{over-damped dynamics} \end{aligned}$$

Underdamped dynamics:


$$\alpha < \omega_0 \text{ or } R/2 < \sqrt{L/C} \quad \text{if } \omega_d \equiv \sqrt{\omega_0^2 - \alpha^2} \text{ then } s_1 = -\alpha + j\omega_d$$


$$s_2 = -\alpha - j\omega_d$$
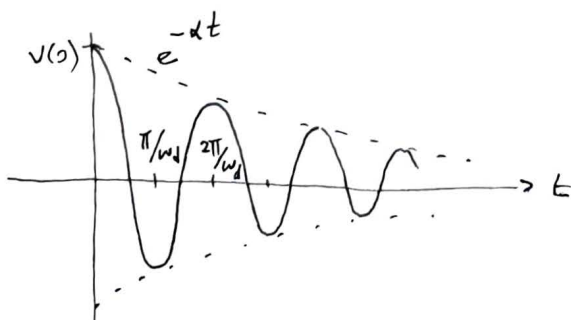
$$\text{and } e^{j\omega_d t} = \cos \omega_d t + j \sin \omega_d t$$



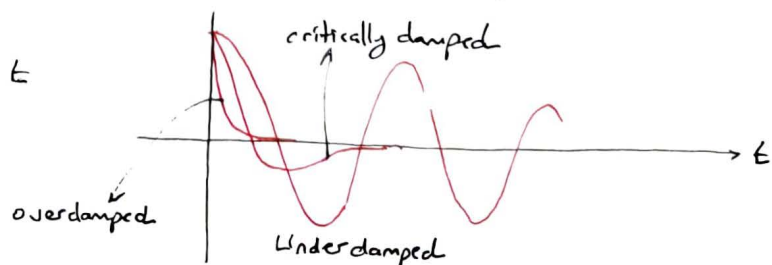if $R=0, \alpha=0$ then signal oscillates forever!



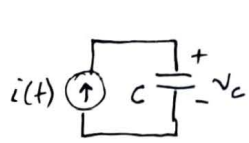* STATE, STATE VARIABLES, COMPUTER SIMULATIONS

$$q(t) = \int_{-\infty}^t i(t) dt$$

This is a memory element. $q(t)$ depends all the ^{past} values. But if we know q at time t_1 , then:

$$q(t_2) = \int_{-\infty}^{t_1} i(t) dt + \int_{t_1}^{t_2} i(t) dt = q(t_1) + \int_{t_1}^{t_2} i(t) dt$$

q is a state variable. Since $q = C \cdot v$, capacitor voltage is a state variable.

Similarly inductor current is a state variable.

State equations are like this:

$$\frac{d}{dt}(\text{state variable}) = f(\text{state variable}, \text{input variable}) \quad \text{if } f \text{ is linear,}$$

$$\frac{d}{dt}(\text{state variable}) = K_1(\text{state var. present value}) + K_2(\text{input variable})$$

Consider



$$i(t) = \frac{v_c}{R} + C \frac{dv_c}{dt} \Rightarrow \frac{dv_c}{dt} = -\frac{v_c}{RC} + \frac{i(t)}{C}$$

v_c is the state variable

Computer analysis:

Recall Euler's method:

$$\frac{dv_c(t)}{dt} \approx \frac{v_c(t+\Delta t) - v_c(t)}{\Delta t} \Rightarrow v_c(t_0 + \Delta t) = v_c(t_0) - \frac{v_c(t_0)}{RC} \Delta t + \frac{i(t_0)}{C} \Delta t$$

Python code: ①

`rc.py`

Solves $\dot{v}_c = -\frac{1}{RC} v_c + \frac{i}{C}$! (Above circuit)

State Equations

$$\dot{x} = Ax + Bu$$

$$y = Cx + Du$$

Python code: ②

Indriven LC circuit

`lc.py`

State equations are derived:

$$\begin{aligned} v &= L \dot{i} \\ i &= C \dot{v} \end{aligned} \Rightarrow \begin{aligned} i(t+\Delta t) &= i(t) + \frac{1}{L} v(t) \Delta t \\ v(t+\Delta t) &= v(t) + \frac{1}{C} i(t+\Delta t) \Delta t \end{aligned}$$