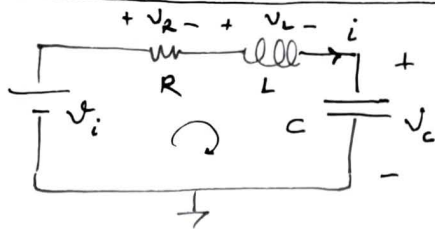


Driven series R-L-C :



$$i = C \frac{d}{dt} v_C(t) \quad \text{or} \quad i = C v_C'(t) \\ v_L = L \cdot i' \Rightarrow v_L = LC v_C''$$

$$\text{KVL: } -v_i + R i + LC v_C'' + v_C = 0$$

$$v_C'' + \frac{R}{L} v_C' + \frac{1}{LC} v_C = \frac{1}{LC} v_i$$

$$\text{or } \frac{d^2}{dt^2} v_C(t) + \frac{R}{L} \frac{d}{dt} v_C(t) + \frac{1}{LC} v_C(t) = \frac{1}{LC} v_i(t)$$

$$v_i(t) = A \cdot u(t) \quad \text{Apply Laplace tr.: } s^2 v_C + \frac{R}{L} s v_C + \frac{1}{LC} v_C = \frac{1}{LC} \cdot \frac{A}{s}$$

$$\Rightarrow v_C(s) = \frac{\frac{A}{LC}}{s^2 + \frac{R}{L}s + \frac{1}{LC}} \Rightarrow v_C(t) = ? \quad (\text{Find using inv. Laplace tr.})$$

State Equations:

$$-v_i + R i + L \frac{di}{dt} + v_C = 0, \quad i = C \frac{dv_C}{dt}$$

$$\frac{di}{dt} = -\frac{R}{L} i - \frac{v_C}{L} + \frac{v_i}{L} \quad \frac{dv_C}{dt} = \frac{i}{C}$$

$$i^+ = i - \frac{R}{L} i \cdot \Delta t - \frac{v_C}{L} \Delta t + \frac{v_i}{L} \Delta t \quad v_C^+ = v_C + \frac{i}{C} \Delta t$$

rlc.py *

$$v_C(t) = K_1 e^{s_1 t} + K_2 e^{s_2 t}, \quad s^2 + 2\alpha s + \omega_0^2 = 0 \quad \text{where } \alpha \equiv \frac{R}{2L} \quad \omega_0 \equiv \frac{1}{\sqrt{LC}}$$

$$\text{the roots are } s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$\text{for } \alpha < \omega_0 \quad s_{1,2} \text{ are complex: } s_1 = -\alpha + j\omega_d \quad \text{where } \omega_d \equiv \sqrt{\omega_0^2 - \alpha^2} \\ s_2 = -\alpha - j\omega_d$$

$$\text{Both oscillatory and decaying behavior: } v_C(t) = A_1 e^{-\alpha t} \cos \omega_d t + A_2 e^{-\alpha t} \sin \omega_d t$$

$$v_C(0) = V_0 + A_1$$

$$i_L(0) = \alpha C A_1 - \omega_d C A_2$$

$$(v_{in}(t) = V_0 u(t)) \\ \text{Step input}$$

$$\text{pg 658: } A_1 = -V_0$$

$$A_2 = -\frac{\alpha}{\omega_d} V_0$$

$$\Rightarrow v_C(t) = V_0 \left(1 - \frac{\omega_0}{\omega_d} e^{-\alpha t} \cos(\omega_d t - \tan^{-1} \frac{\alpha}{\omega_d}) \right) u(t)$$

$$i_L(t) = -\frac{V_0}{\omega_d L} e^{-\alpha t} \sin \omega_d t u(t)$$

* Write python code to simulate driven parallel R-L-C circuit:



$$\text{Plot } i_R, i_L, i_C. \quad v_i(t) = 10 u(t)$$

$$= 10 \sin \omega t$$

$$= 10 t u(t)$$


⋮

HIGHER ORDER CIRCUITS/SYSTEMS


5

Analogy with mechanical systems:

Electrical	Mechanical
Current (i)	Force (f)
voltage (v)	velocity (v)
resistance (r)	lubricity ($1/B$) (inv. friction)
capacitance (c)	mass (m)
inductance (L)	compliance ($1/k$) (inv. spring)

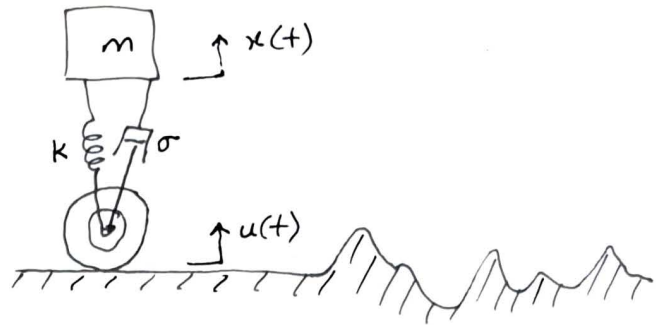

$$\sum f = 0$$


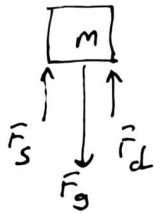


$$F_g = mg$$

$$F_s = k(x - u)$$

$$F_d = \sigma(\dot{x} - \dot{u})$$

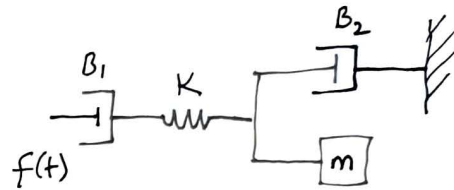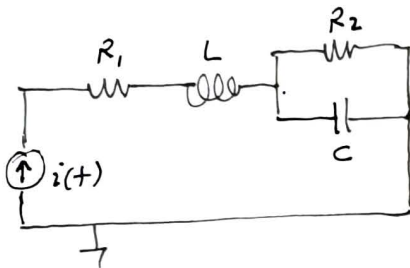
$$\Rightarrow m\ddot{x} + \sigma\dot{x} + kx = ku + \sigma\dot{u}$$



* Find the resonant frequency for undriven LC, or spring-mass:

$$\text{we know that } \omega_0 = \frac{1}{\sqrt{LC}} \rightsquigarrow \omega_0 = \sqrt{\frac{k}{m}}$$

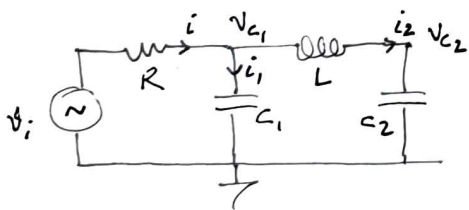Third-order circuit (Low-pass filter application)



$$i = i_1 + i_2$$

$$i_1 = C_1 \frac{dv_{c1}}{dt}$$

$$i_2 = C_2 \frac{dv_{c2}}{dt}$$

$$v_i - v_{c1} = R(i_1 + i_2) \Rightarrow i_1 = \frac{v_i}{R} - \frac{v_{c1}}{R} - i_2$$

$$v_{c1}' = \frac{i_1}{C_1}, \quad v_{c2}' = \frac{i_2}{C_2}$$

$$L i_2' = v_{c1} - v_{c2} \Rightarrow i_2' = \frac{1}{L}(v_{c1} - v_{c2})$$

- write state equations

- simulate circuit with `rc1lc2.py`

for v_i :

1) step input

2) ramp input

3) $\sin(\omega t)$ for different ω values.

4) a noisy $\sin(\omega t)$ to observe filter effect.

play with L, C values to see cut-off frequency and phase difference!

Recall:

$$\omega = 2\pi f$$