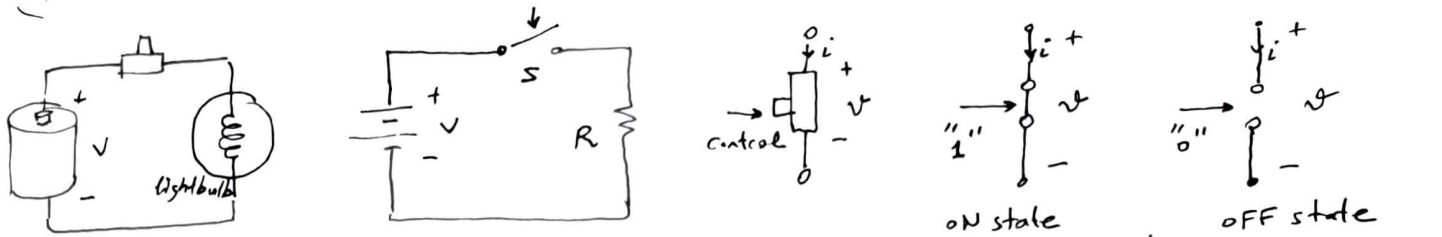



MOSFET SWITCH / AMPLIFIER

①




(Metal oxide Semiconductor Field Effect Transistor)




Logic functions using Switches:

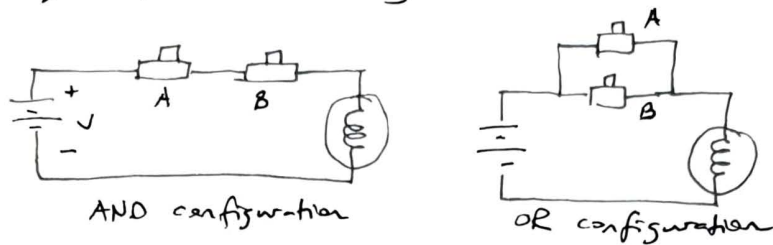

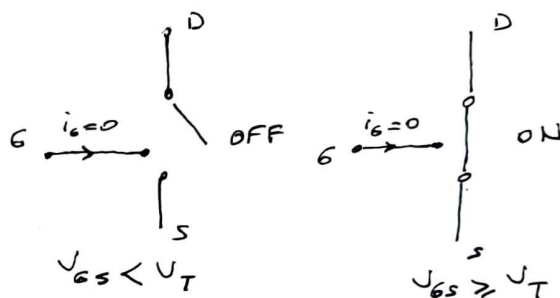
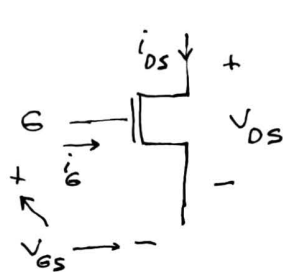
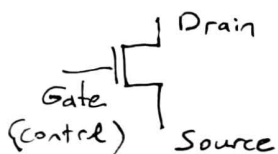
MOSFET is a type of transistor that is three-terminal device:




S-Model (Simple switch model)

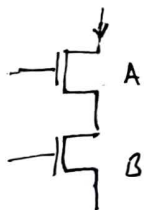


AND

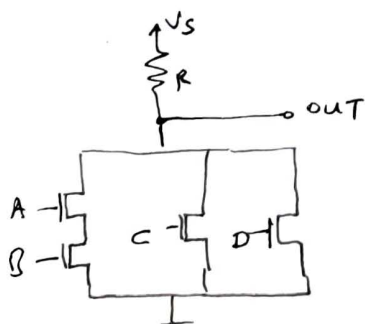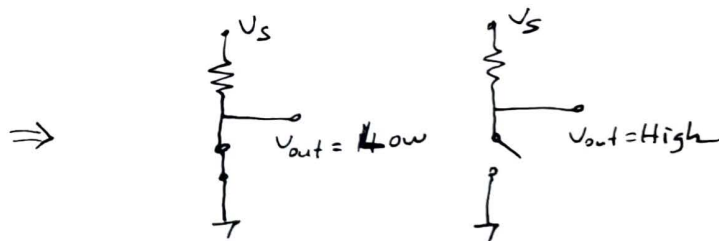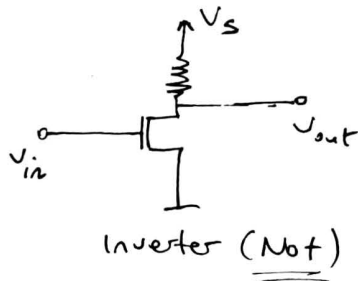


$$f = AB + C + D$$

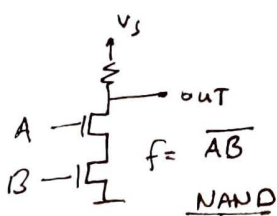

$$f = \overline{AB}$$

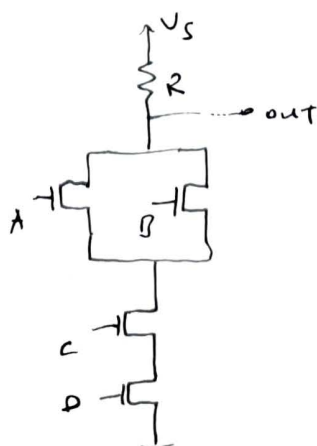



$$f = (A+B)CD$$

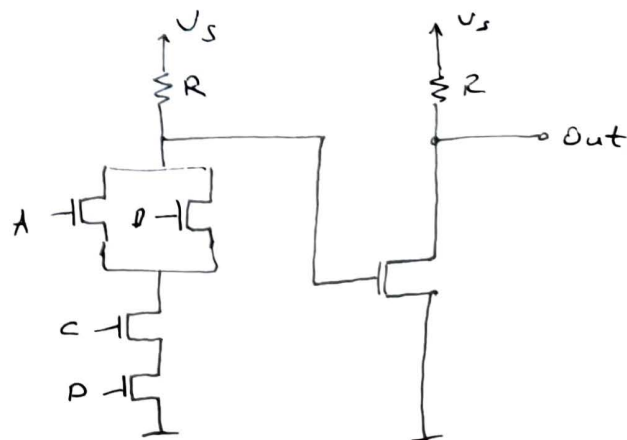



$$f = (A+B)C D$$

MOSFET - Signal Amplification

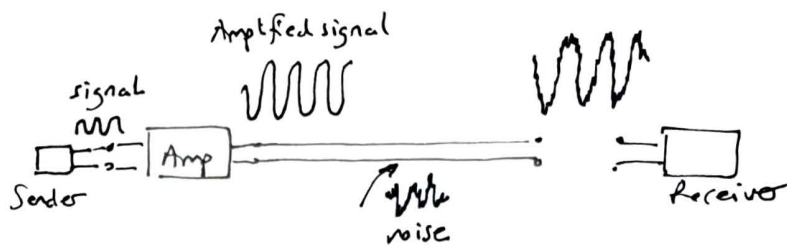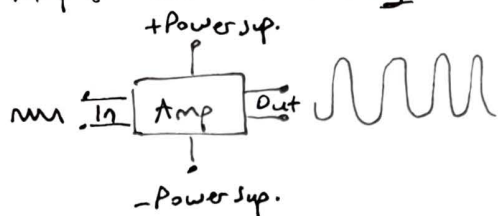Amplification is a ~~key~~ kind of signal processing.



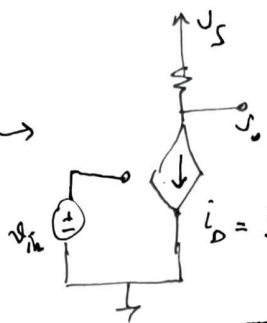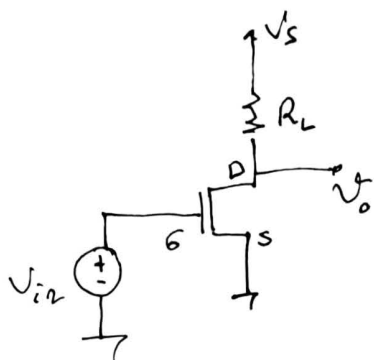
- a) Amplification provides noise-tolerance!
- b) " is needed for low-output sensors before Analg-to-Digital conversion.



$$V_{GS} = V_{in} \\ V_{DS} = V_o \\ i_{DS} = \frac{K(V_{GS} - V_T)^2}{2} \\ \text{and } i_D = \frac{V_S - V_o}{R_L}$$

Therefore $V_o = V_S - \frac{K(V_{in} - V_T)^2}{2} \cdot R_L$

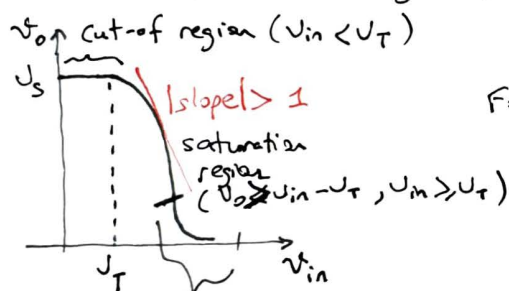The transfer function (or gain) is : $\frac{V_o}{V_{in}} = \frac{V_S - K(V_{in} - V_T)^2 \cdot R_L / 2}{V_{in}}$ (non linear)




For ex : $V_S = 10V$
 $K = 1mA/V^2$
 $R_L = 10k\Omega$
 $V_T = 1V$

$\Rightarrow V_o = 10 - 5(V_{in} - 1)^2$

V_{in}	V_o	
1	10	→ Cut-off
1.4	9.2	} Saturation region (Good for amplifying)
1.5	8.8	
1.8	6.8	
1.9	6	
2	5	
2.1	4.0	
2.2	2.8	} Triode region $V_{in} > 2.3$
2.3	1.6	
2.32	1.3	
2.35	0.9	
2.4	~0	

Bipolar Junction Transistor (BJT)

3

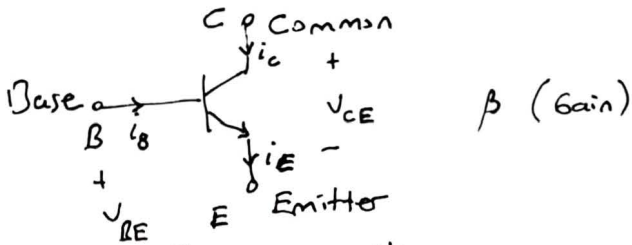

Determine V_o for $V_{in} = 1V, 1.1V, 1.2V$
 $(R_I = 100k\Omega, R_L = 10k\Omega, \beta = 100, V_S = 17V)$

$$i_B = \frac{V_{in} - 0.6}{R_I} \quad \text{and} \quad \frac{V_S - V_o}{R_L} = \beta i_B$$

$$V_o = V_S - \frac{V_{in} - 0.6}{R_L} \cdot \beta \cdot R_L = 16 - 10V_{in}$$

$$V_{in} = 1V \Rightarrow V_o = 6V$$







$$V_{in} = 1.1V \Rightarrow V_o = 5V$$

$$V_{in} = 1.2V \Rightarrow V_o = 4V$$

$$V_{in} = 1.2V, V_o = 4V \Rightarrow V_{BC} = V_{BE} - V_{CE} = 0.6 - 4 = -3.4 < 0.4 \text{ (threshold)}$$

$$V_{CE} > 0.2 \text{ (threshold)}$$

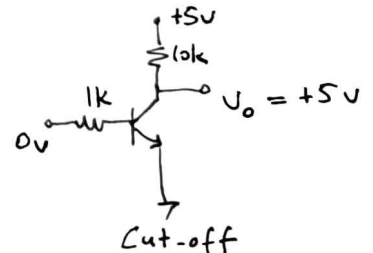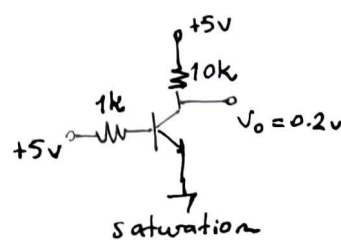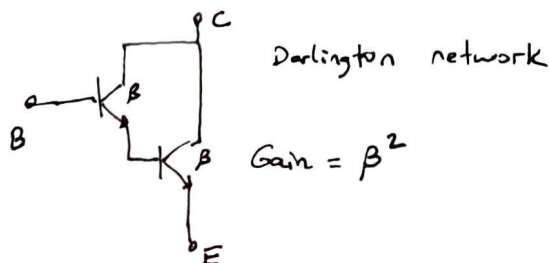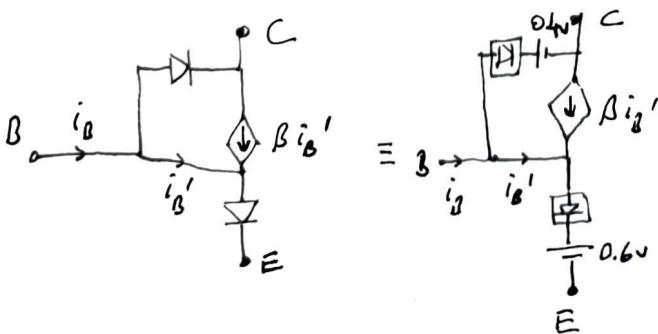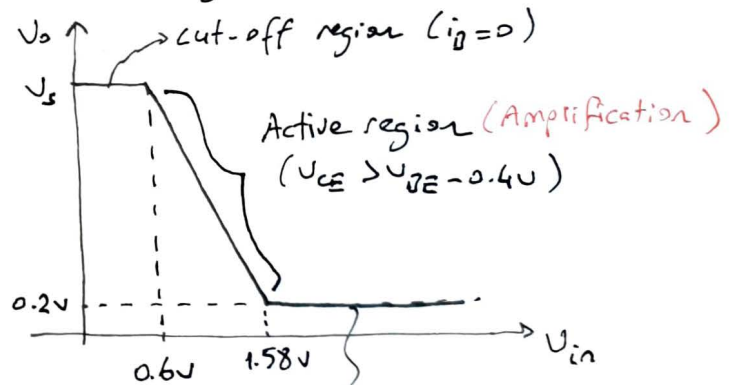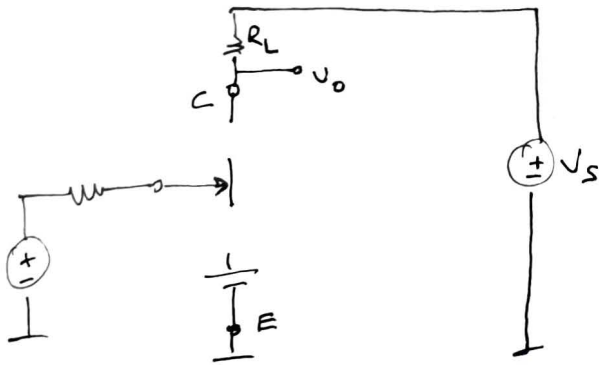We can conclude that transistor is in active region.



This is a NOT gate!