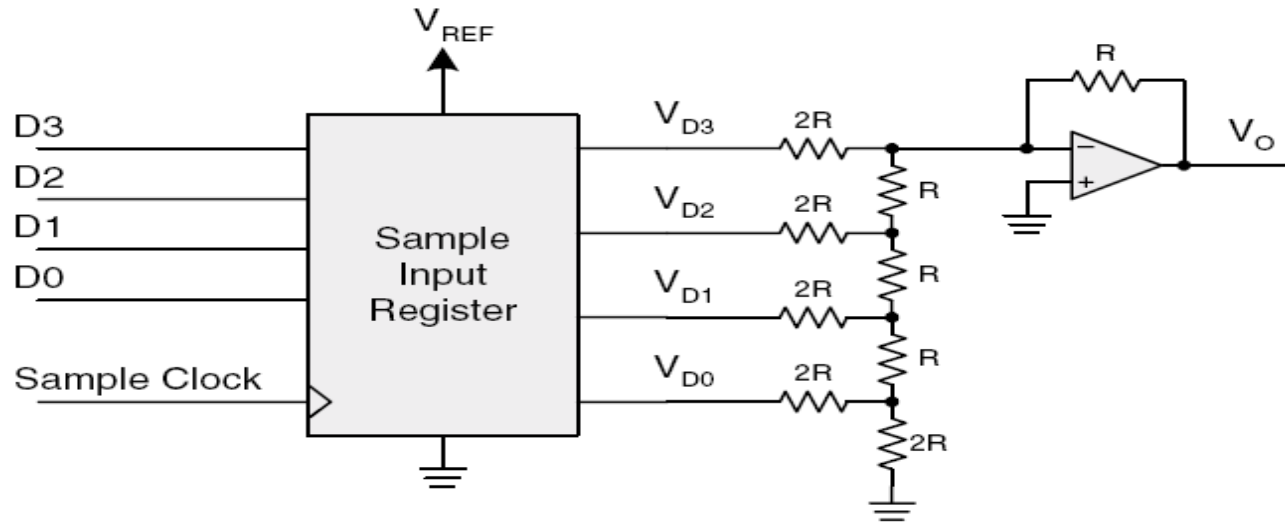


Data conversion:
ADC / DAC

Digital-to-Analog Converter (DAC)



$$V_O = -V_{REF} \left[\frac{D3}{2} + \frac{D2}{4} + \frac{D1}{8} + \frac{D0}{16} \right]$$





Analog-to-Digital Conversion

Analog-to-digital conversion (ADC) and digital-to-analog conversion (DAC) are the processes that allow digital computers to interact with everyday signals: voltage, current, distance, velocity, temperature, altitude, force, acceleration, pressure etc.





Digital information is different from its analog counterpart in two respects:

- it is sampled
- it is quantized


ADC Principles: S/H and Quantization

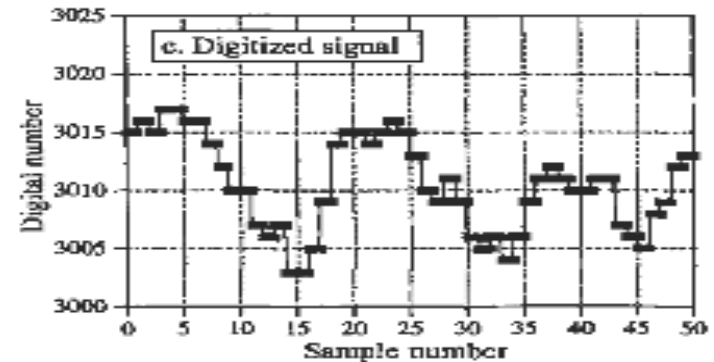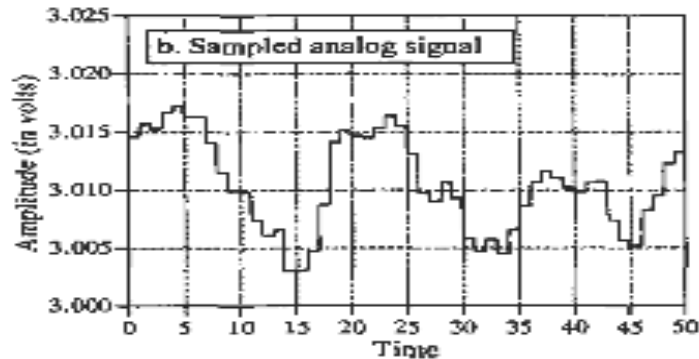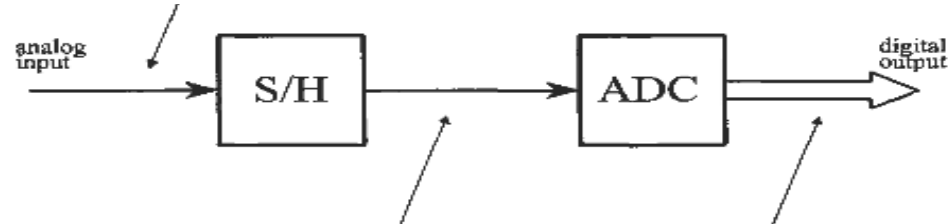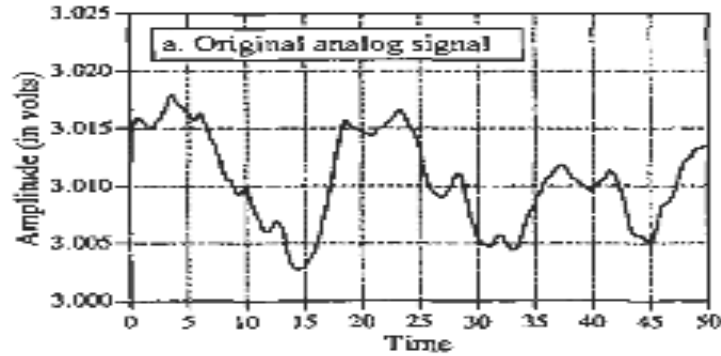

Quantization Error

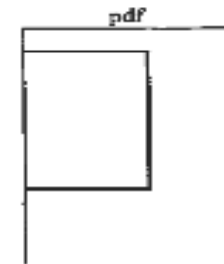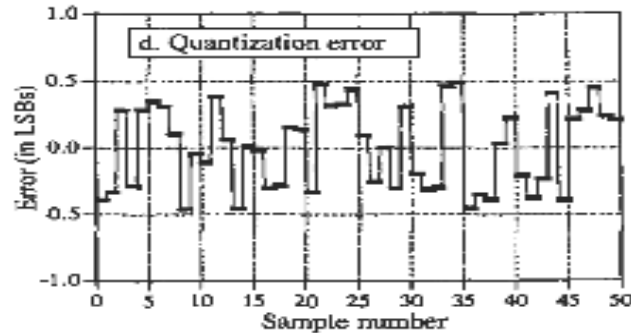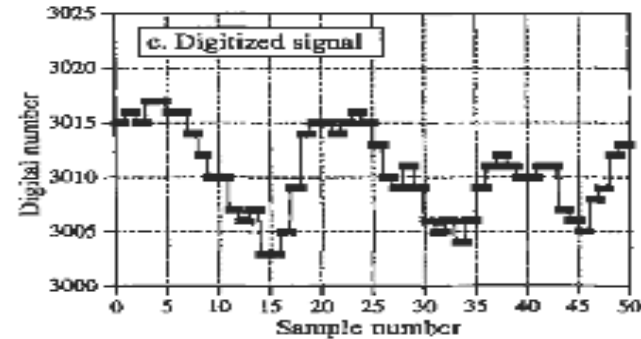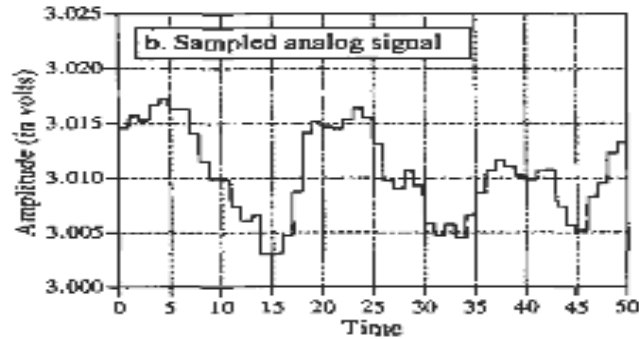

A 1-bit ADC

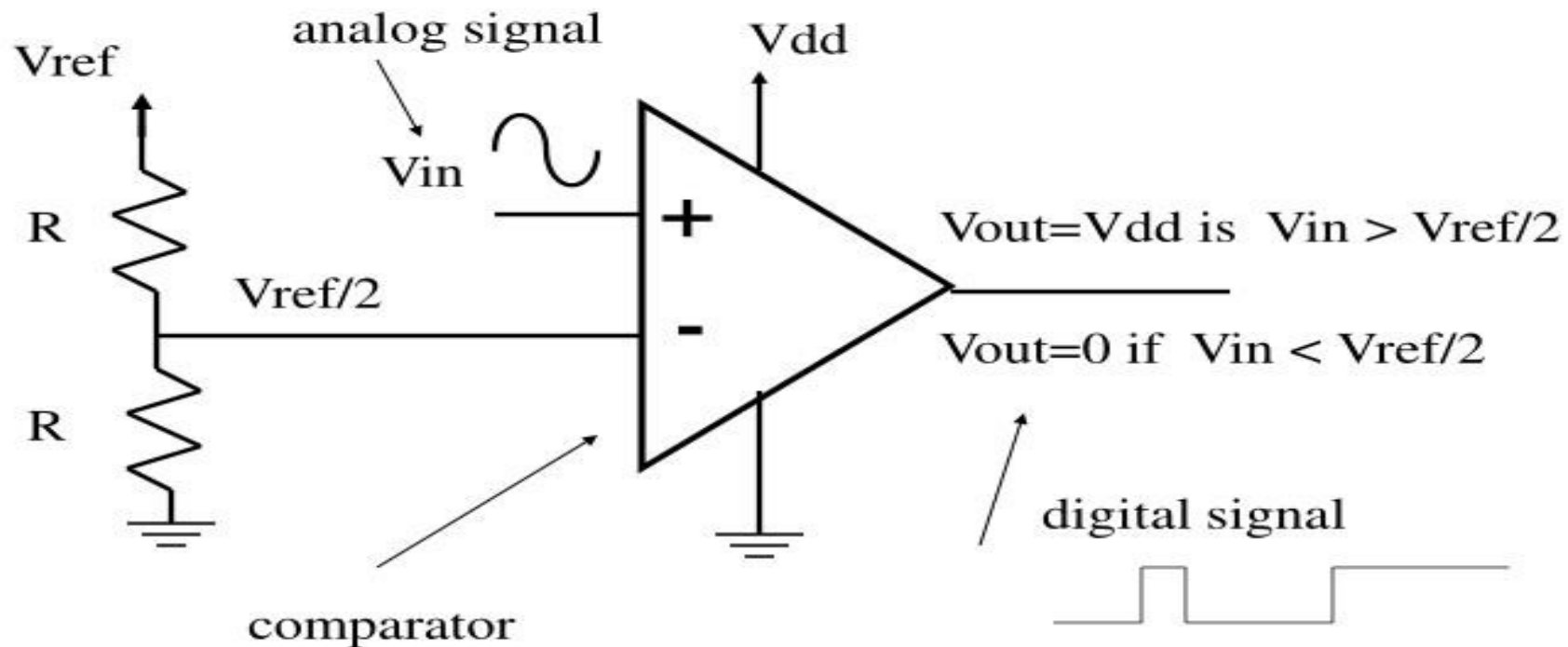

1-bit ADC

- Analog signal range: 0 – 5 v
- $V_{ref} = 2.5 \text{ v}$
- $V_{dd} = 5 \text{ v}$

V_{in} : 0 – 2.5 v --> V_{out} : 0 v (FALSE)

V_{in} : 2.5 – 5 v --> V_{out} : 5 v (TRUE)


Resolution: 2

Example:


$V_{in} = 3.8 \text{ v}$

- What is the output of 1-bit ADC?
- What is the quantization error?

Analog-to-Digital Conversion

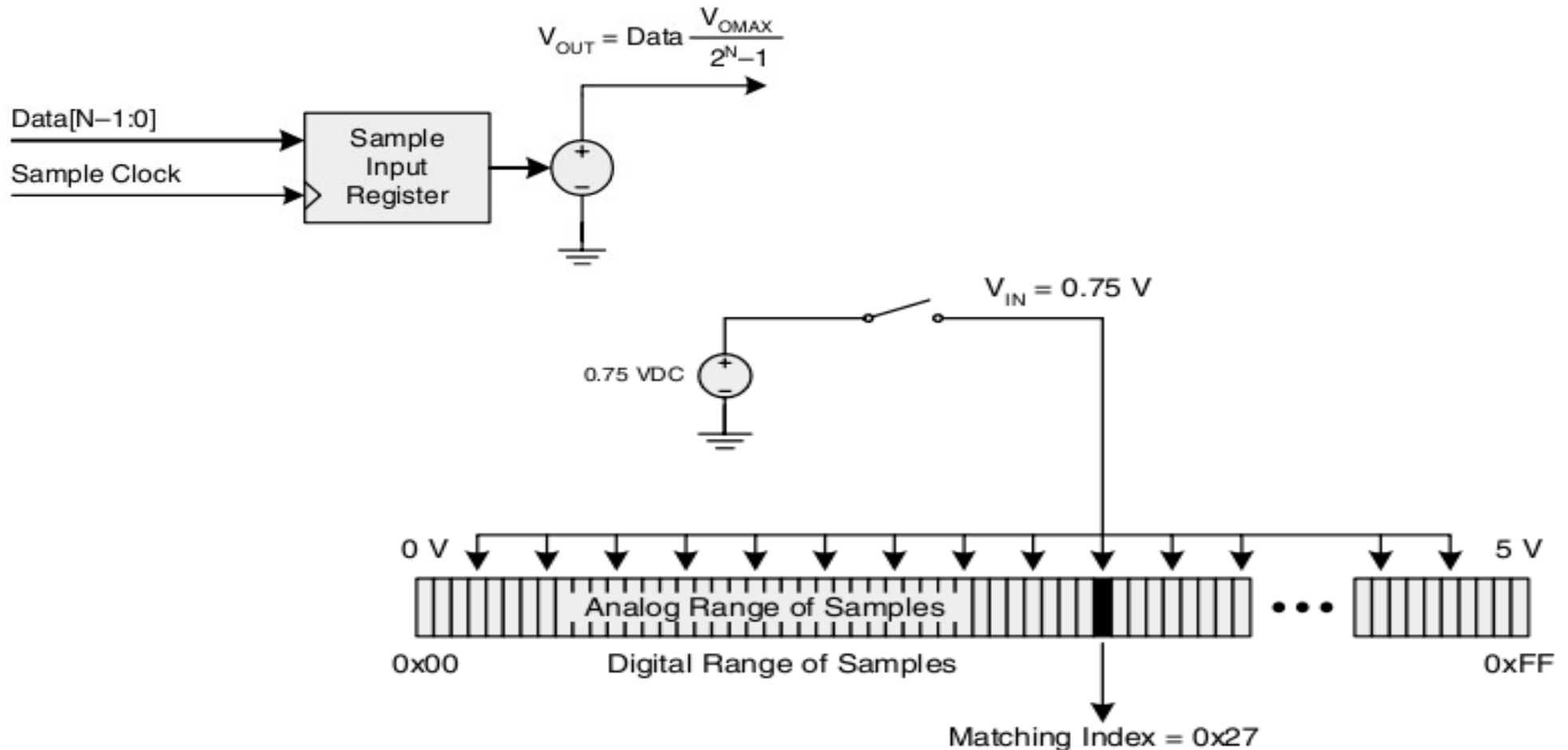





Sampling Theory

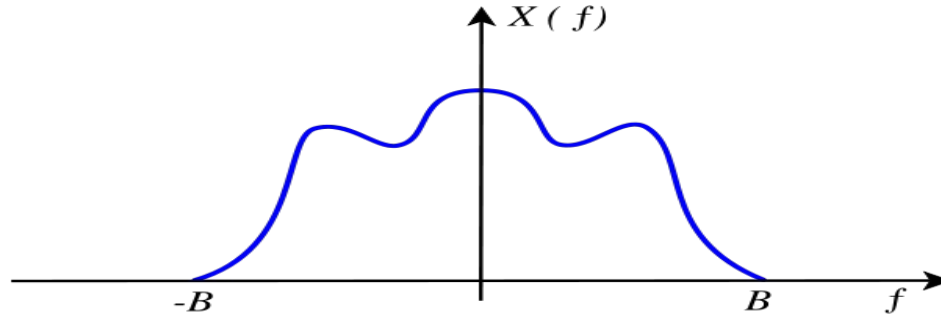

Nyquist theorem:

Analog signal that has been digitized can be perfectly reconstructed if the sampling rate was $1/(2W)$ seconds, where W is the highest frequency in the original signal.


Sampling Theory

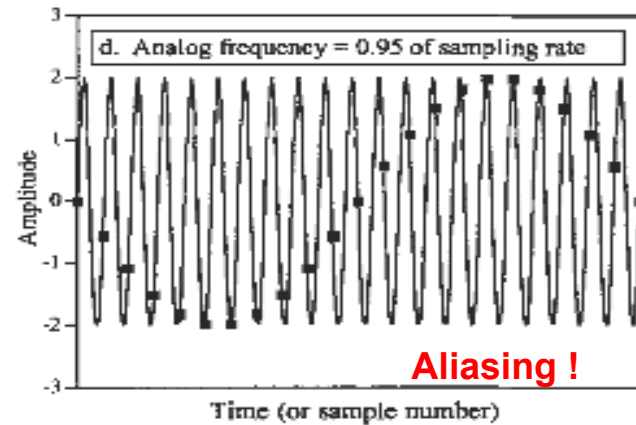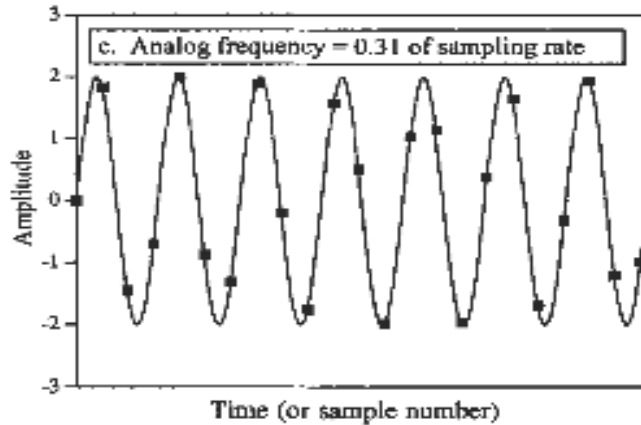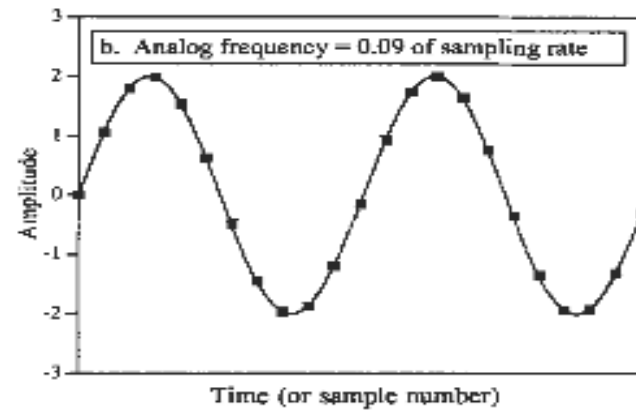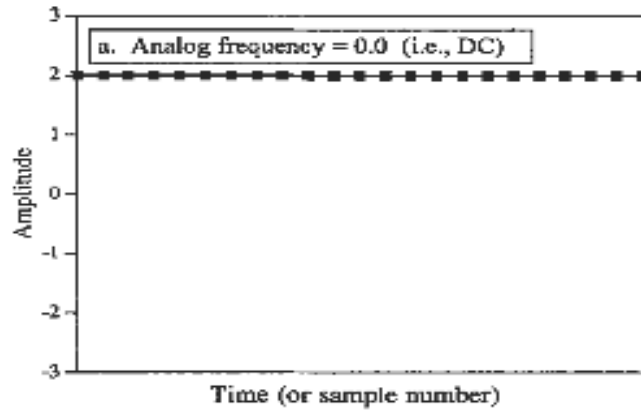


1. *Run adc.py*

2. *Evaluate the ADC with different parameters and discuss*

Using Analog Filters

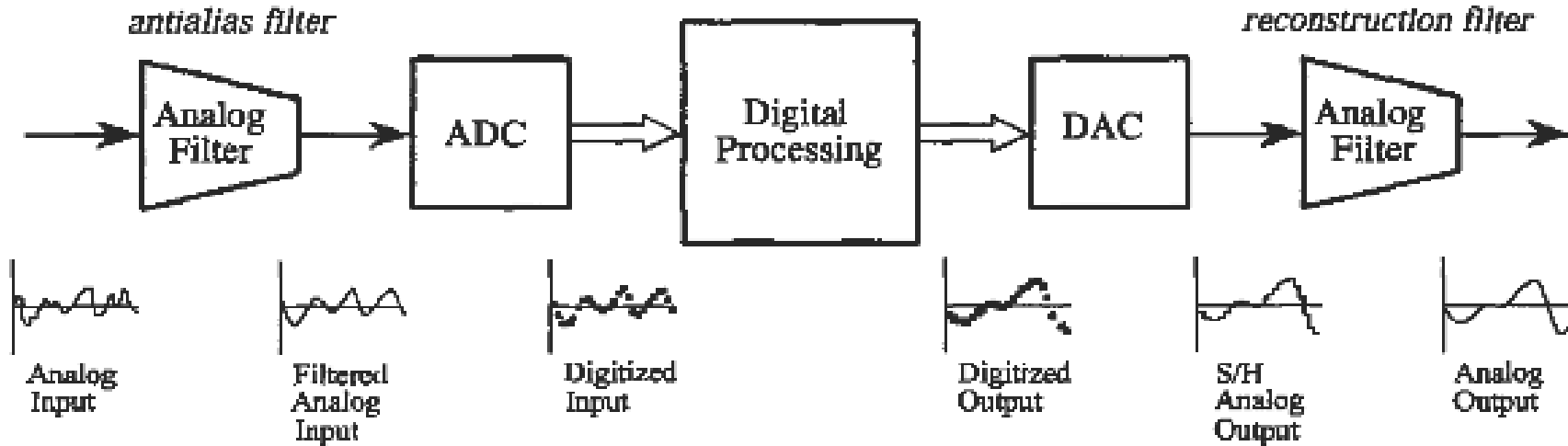



Basic A/D Architecture

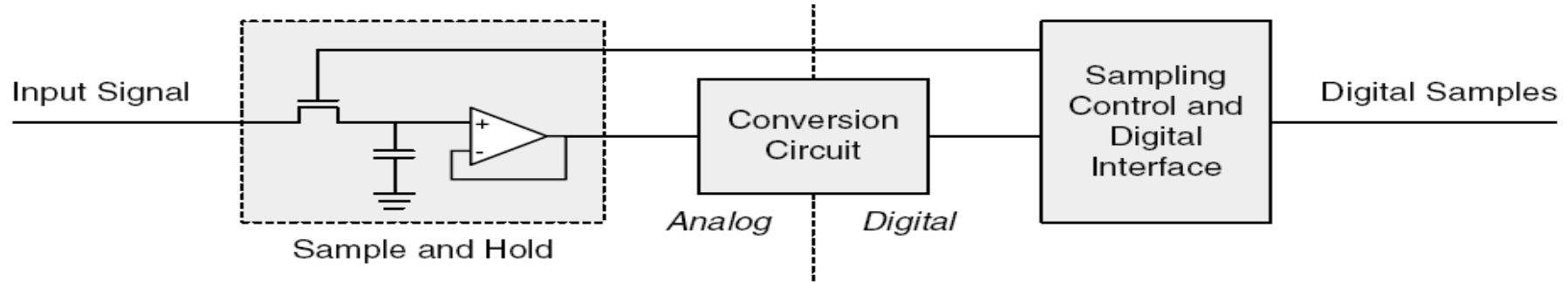

ADC Types:


- Ramp ADC
- Flash ADC
- Successive-approximation ADC
- Sigma-delta ADC

Ramp ADC

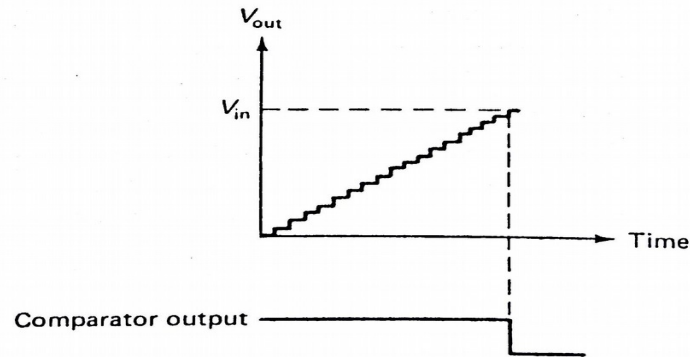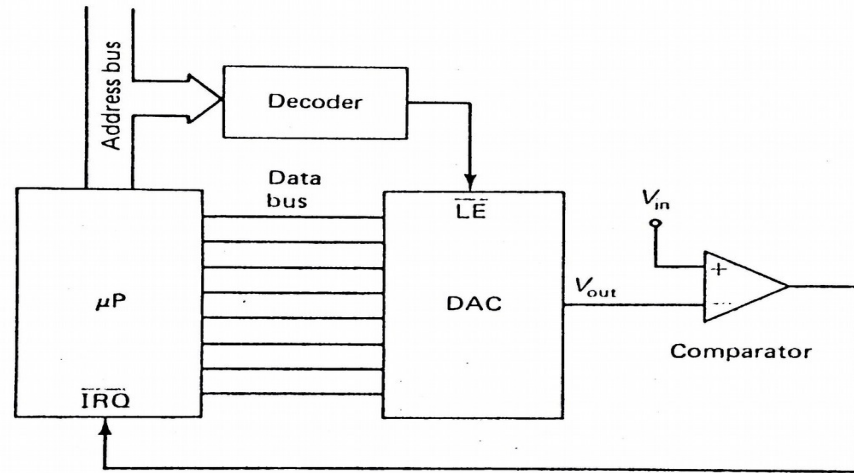


n-bit ADC requires 2^n cycles to perform a conversion in worst case.

Flash ADC

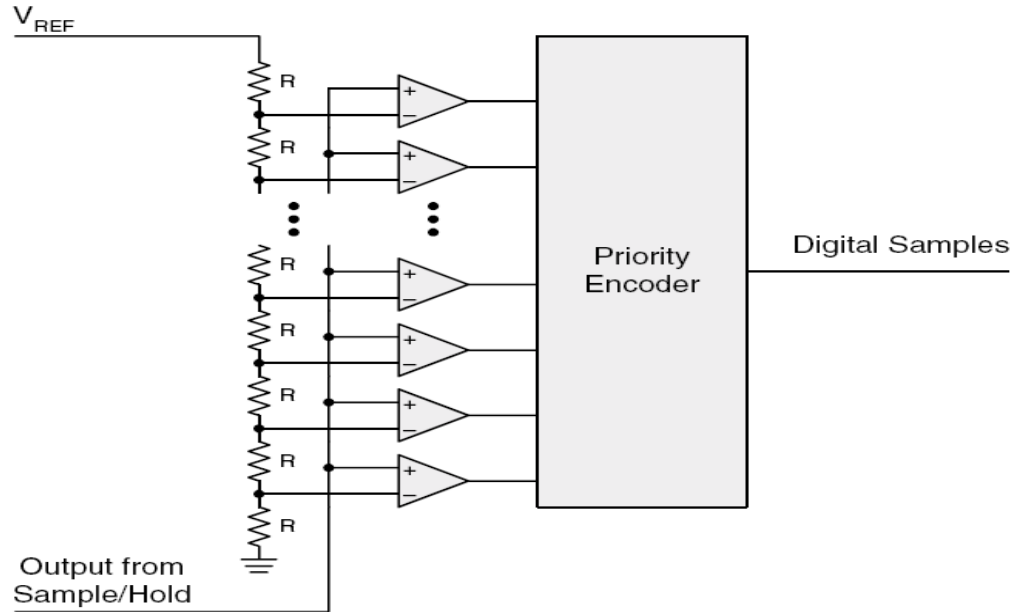



- Requires 4095 parallel comparators for 12-bit.
- Very fast, conversion is done in one step.
- Complexity doubles with each added bit of resolution.

Successive-approximation ADC

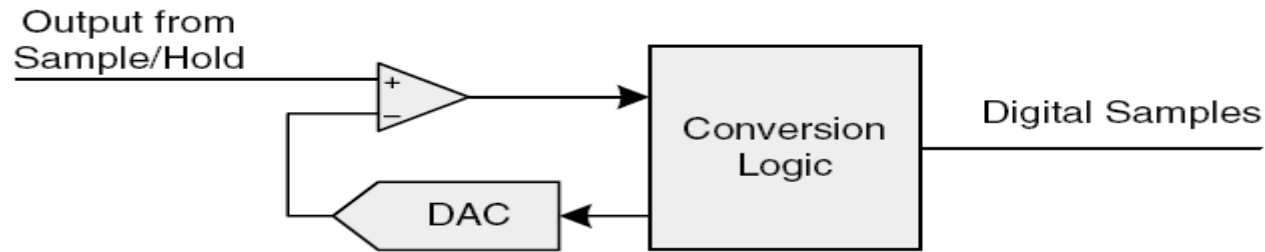


- Uses an internal n-bit DAC
- Conversion logic is a simple n-bit counter
- n-bit ADC requires n cycles to perform a conversion
in worst case.

Successive Approximation Conversion

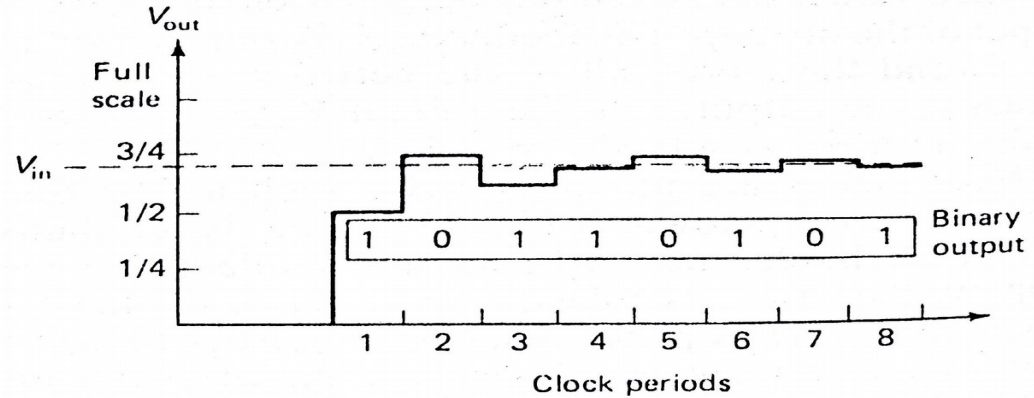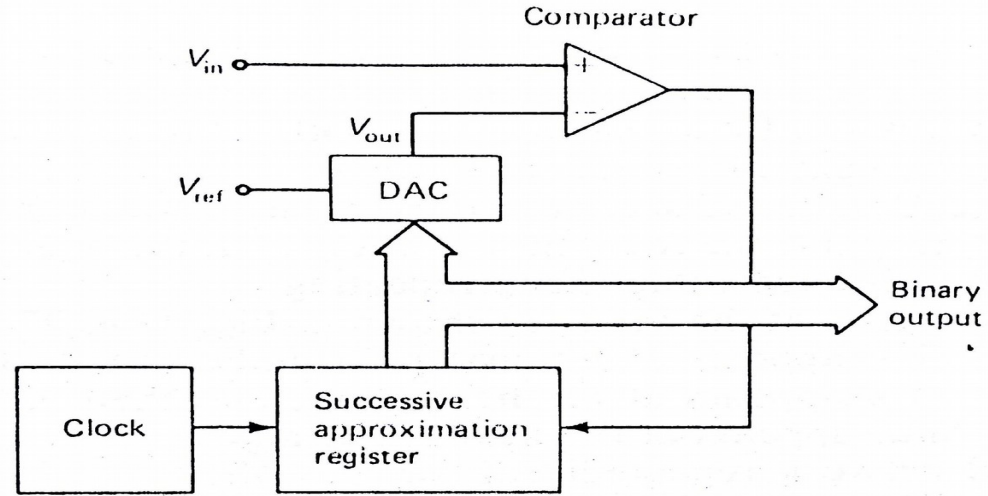

Delta-sigma ADC

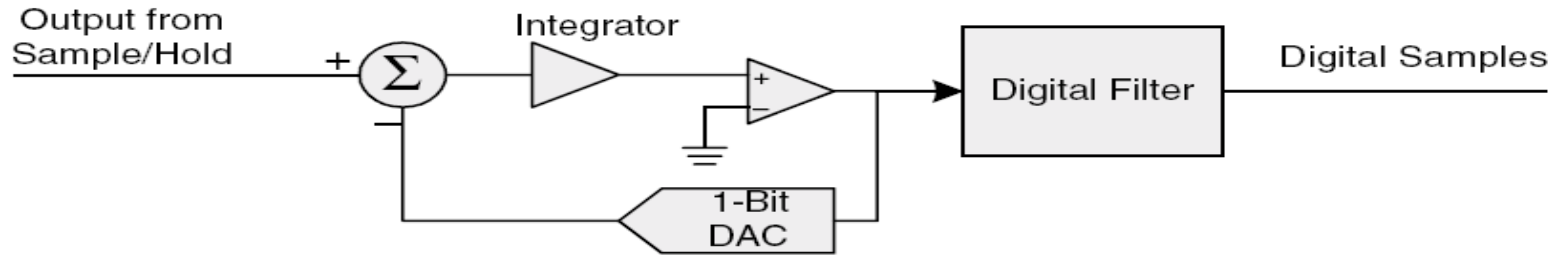

- Requires 1-bit DAC: less susceptible to noise
- Requires high sampling rate, suitable for audio applications
- It has digital filter, so no need for expensive low-pass filters at input
- Resolution can be very high.

NE5034 ADC

