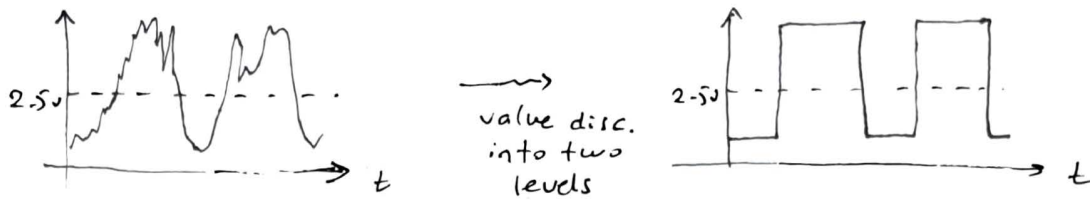


DIGITAL ABSTRACTION

①/1

Based on value discretization. The idea is to lump signal values that fall within some interval into a single value.




Analog signal is a real function $f: \mathbb{R} \rightarrow \mathbb{R}$ that describes the voltage of a given point as a function of time. Signal is a continuous function.

Digital function is defined as $g: \mathbb{R} \rightarrow \{0, 1, \text{non-logical}\}$




$$\text{Simply: } \text{dig}(f(t)) \triangleq \begin{cases} 0 & \text{if } f(t) < V' \\ 1 & \text{if } f(t) \geq V' \end{cases}$$

To eliminate the noise effect at $f(t)$ around V' , we put a gap:
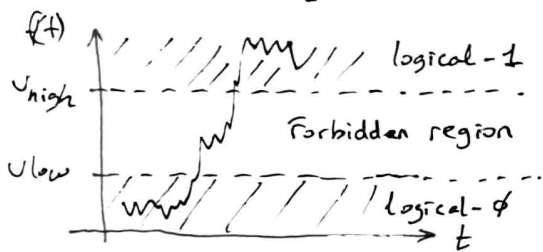
$$\text{dig}(f(t)) \triangleq \begin{cases} 0 & \text{if } f(t) < V_{\text{low}} \\ 1 & \text{if } f(t) > V_{\text{high}} \\ \text{non-logical} & \text{otherwise} \end{cases} \quad V_{\text{low}} < V_{\text{high}}!$$



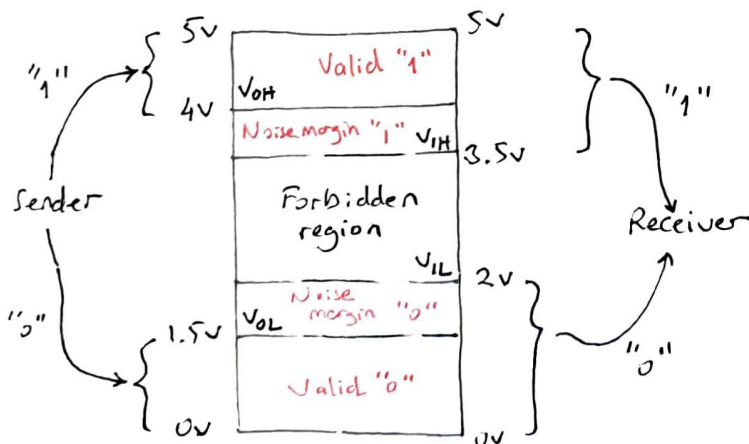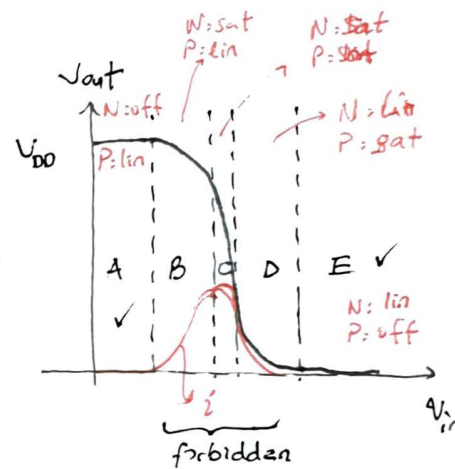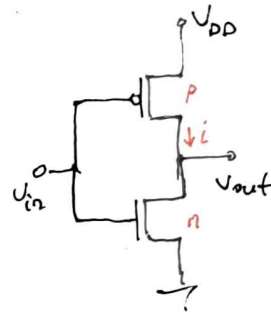Using CMOS invert gate
MOSFET transistors




Gate Abstraction




Gates: AND OR NOT ...



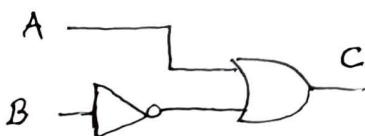The gate-level digital circuit for Boolean expression $C = A + \bar{B}$:



Analyse this circuit:

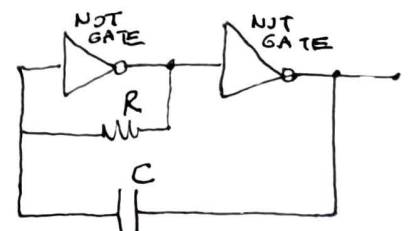

Continue next: ADC.ppt

Run adc.py