

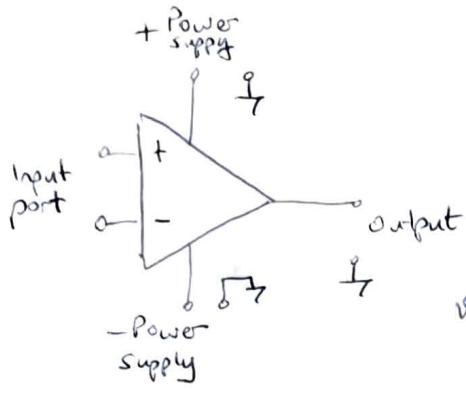


OPAMP (Operational Amplifier) Abstraction

(1)

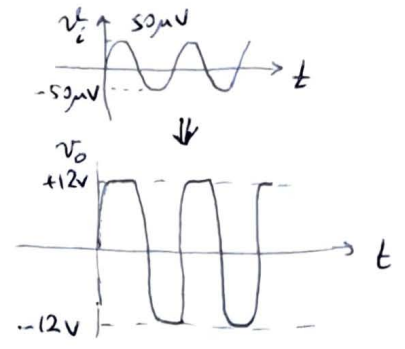


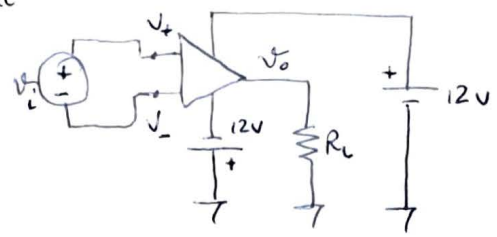It's an important device for electronic circuit design. Four-port device. The input impedance is too high, the output impedance is too low. The gain is about 300,000 etc.



The gain is too high and unreliable. Generally used with feedback.

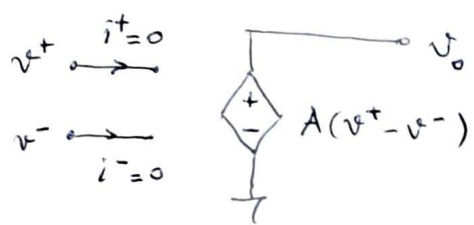The idealized opamp (voltage controlled voltage source) is as follows:




$$v_o = A(v^+ - v^-)$$

$$A \rightarrow \infty$$

$i^+ = i^- = 0 \Rightarrow$ input resistance is infinite.

The output resistance is 0.

Non-inverting opamp: (Negative feedback)

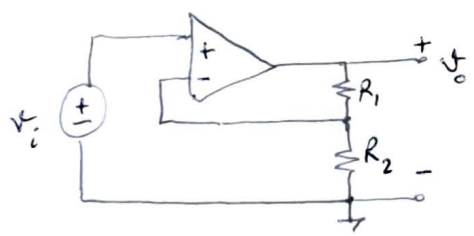


$$v^+ = v_i$$

$$\frac{v^-}{R_2} + \frac{v^- - v_o}{R_1} = 0 \quad \text{or} \quad v^- = \frac{R_2}{R_1 + R_2} v_o$$

$$v_o = A(v^+ - v^-) \Rightarrow v_o = A v_i - A v^-$$



The model:

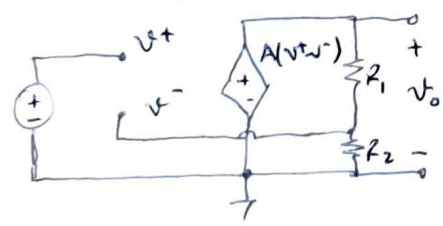

$$v_o + A \cdot \frac{R_2}{R_1 + R_2} v_o = A v_i \Rightarrow v_o = \frac{A v_i}{1 + A \frac{R_2}{R_1 + R_2}}$$

$$\lim_{A \rightarrow \infty} v_o = \left(1 + \frac{R_1}{R_2}\right) v_i$$

Inverting connection:

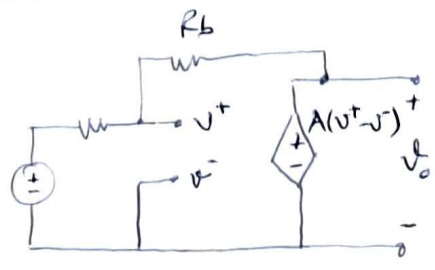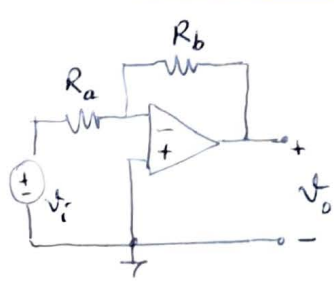

$$v^+ = 0$$

$$\frac{v_i - v^-}{R_a} + \frac{v_o - v^-}{R_b} = 0$$


$$v_o = A(v^+ - v^-)$$

$$\Rightarrow v_o = \frac{-AR_b / (R_a + R_b)}{1 + AR_a / (R_a + R_b)} \cdot v_i$$

$$\lim_{A \rightarrow \infty} v_o = -\frac{R_b}{R_a} \cdot v_i$$

OPAMP

The voltage follower :

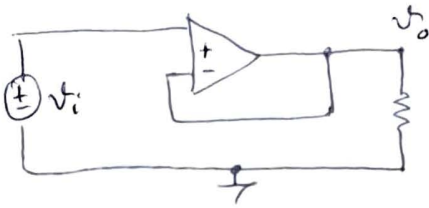


$$v_o = A(v_i - v_o)$$

$$v_o(A+1) = A v_i$$

$$v_o = \frac{A v_i}{1+A} \Rightarrow \lim_{A \rightarrow \infty} v_o = v_i$$

The current source :

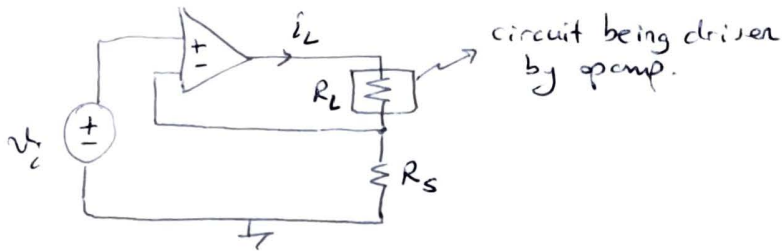


$$v^+ = v_i$$

$$v^- = i_L R_s$$

$$v^+ \approx v^- \Rightarrow i_L \approx \frac{v_i}{R_s}$$

(independent of load, R_L)

Adder :

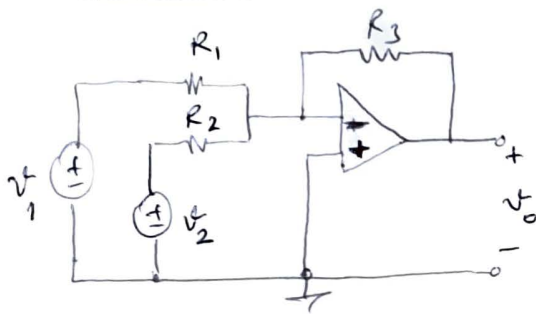


$$\text{KCL @ } v^- : \frac{v_1}{R_1} + \frac{v_2}{R_2} + \frac{v_o}{R_3} \approx 0$$

$$v^+ = 0 \approx v^-$$

$$v_o \approx - \left(\frac{R_3}{R_1} v_1 + \frac{R_3}{R_2} v_2 \right)$$

Subtractor :

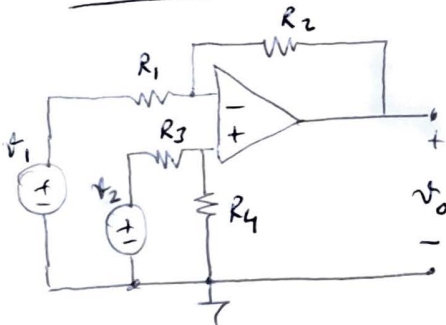


$$v^+ = \frac{v_2}{R_3 + R_4}, R_4 = a \quad \frac{v^+ - v_1}{R_1} + \frac{v^+ - v_o}{R_2} = 0$$

$$R_2(a v_2 - v_1) + R_1(a v_2 - v_o) = 0$$

$$v_o = a \left[\frac{R_2(v_2 - v_1) + R_1 v_2}{R_1} \right]$$

$$v_o = \left(\frac{R_3}{R_3 + R_4} \right) \left(\frac{R_1 + R_2}{R_1} v_2 - \frac{R_2}{R_1} v_1 \right)$$

$$\text{Taking } R_3 = R_1, R_4 = R_2 \Rightarrow v_o = \frac{R_2}{R_1} (v_2 - v_1)$$



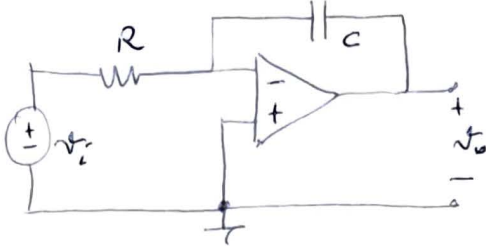
Opamp Integrator

$$\frac{v_i - v^-}{R} + C \frac{d(v_o - v^-)}{dt} = 0$$

$$v^+ \approx v^- \Rightarrow v^+ = 0$$




$$\frac{v_i}{R} + C \frac{dv_o}{dt} = 0$$

$$v_o \approx -\frac{1}{RC} \int v_i dt$$

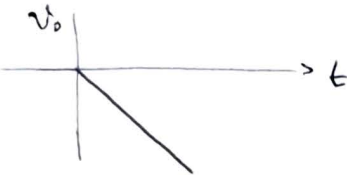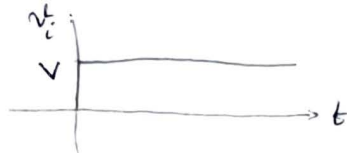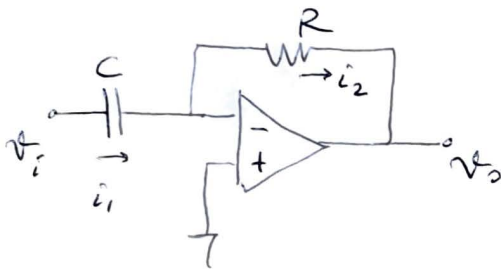
Opamp Differentiator

$$i_1 = C \frac{dv_i}{dt} \quad v_o = -R i_1 \quad (i_1 = i_2)$$

$$v_o = -RC \frac{dv_i}{dt}$$

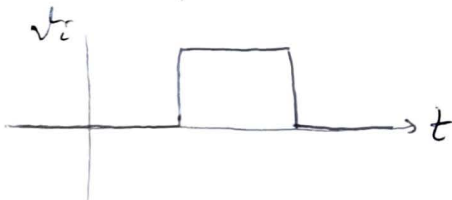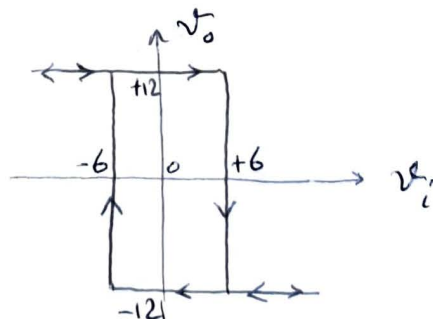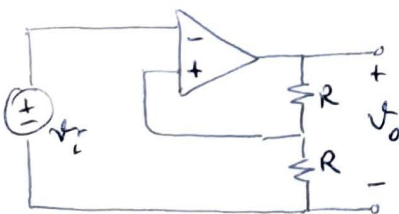Positive Feedback :




Opamp works in saturation regions and shows hysteresis.

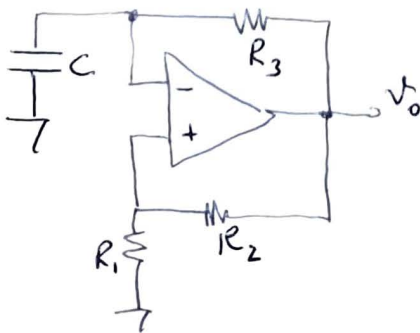RC Oscillator :

(4)

OPAMP

RC-oscillator cont'd 2

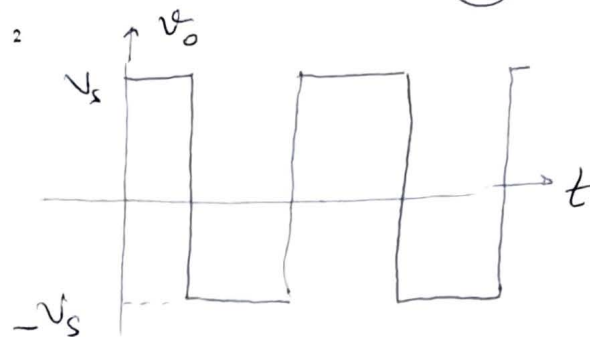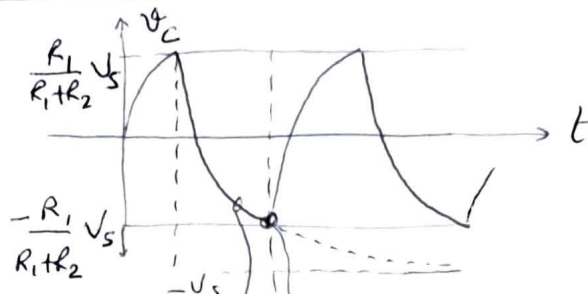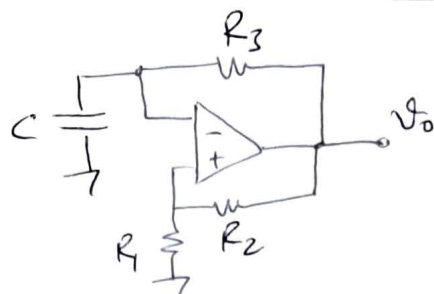

$$V_c = -V_s + \left(\frac{R_1}{R_1 + R_2} + 1 \right) V_s e^{-t/R_3 C} \quad \left(\begin{array}{l} V_c(0) = V_s \frac{R_1}{R_1 + R_2} \\ V_c(\infty) = -V_s \end{array} \right)$$

find this time: T_{Low} :

$$V_c = -V_s + \left(\frac{R_1}{R_1 + R_2} + 1 \right) V_s e^{-t/R_3 C} \leq -\frac{R_1}{R_1 + R_2} V_s$$

$$-V_s + \left(\frac{R_1}{R_1 + R_2} + 1 \right) V_s e^{-T_{Low}/R_3 C} = -\frac{R_1}{R_1 + R_2} V_s$$

$$\Rightarrow T_{Low} = R_3 C \ln \left(1 + \frac{2R_1}{R_2} \right)$$

$$T_{High} = T_{Low}, \text{ so } T = 2R_3 C \ln \left(1 + \frac{2R_1}{R_2} \right)$$