

CENG 311

Computer Architecture

Lecture 4


Single and General Purpose μ P Design

Design of the Components: Datapath and Control Unit


Asst. Prof. Tolga Ayav, Ph.D.

Department of Computer Engineering
İzmir Institute of Technology

General Structure of a Microprocessor

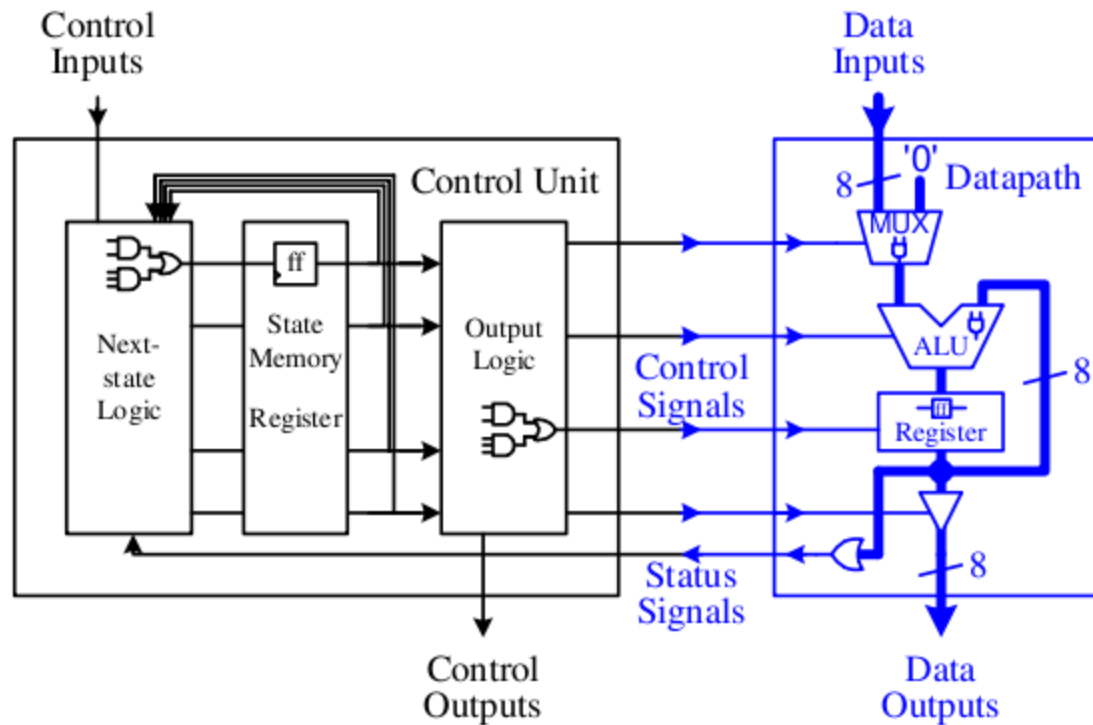

Overview of CPU Design

 


Datapath


- Manipulates data. It includes:
 - Functional units: Adder, shifter, multiplier, ALU, comparator
 - Registers and other memory elements for the temporary storage of the data
 - Buses, multiplexers and tri-state buffers for the transfer of data between the different components in datapath and the external world.

Why do we use datapath?

 - how do we design a circuit for performing more complex data operations or operations that involve multiple steps?



 combinational circuit to add four numbers;




datapath to add one million numbers.

Designing Deticated Datapaths


- What kind of registers to use, and how many are needed?
- What kind of functional units to use, and how many are needed?
- Can a certain functional unit be shared between two or more operations?
- How are the registers and functional units connected together so that all of the data movements specified by the algorithm can be realized?

Two sample dedicated datapaths


$$A = A + 3$$

 


$$A = B + C$$

 

Use of multiplexers

 

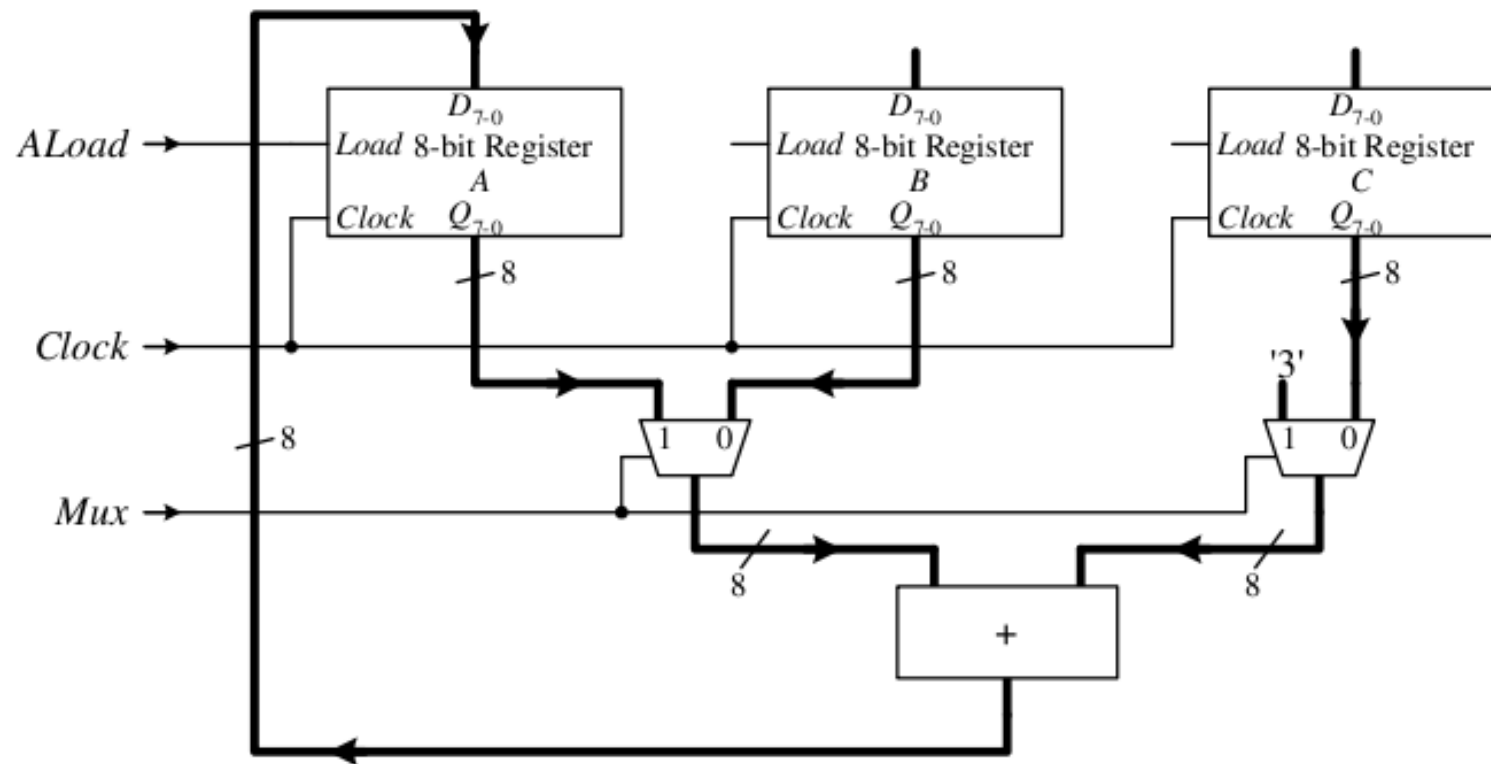Datapath performing both $A = A + 3$ and $A = B + C$ (we use two adders).





Datapath performing both $A = A + 3$ and $A = B + C$ (we use only one adder).

Data Transfer


Multiple destinations is not a problem. We can connect all of the destinations to the same source (**Pay attention to the fan-out**).

  In case of multiple sources, multiplexers are used.





Tri-state Bus

 Another scheme where multiple sources and destinations can be connected to the same data bus is through the use of tri-state buffers.




Generating Status Signals

  Status signals are the results of the conditional tests that the datapath supplies to the control unit.



Example: Generating Status Signals

IF (A is an odd number) THEN ...

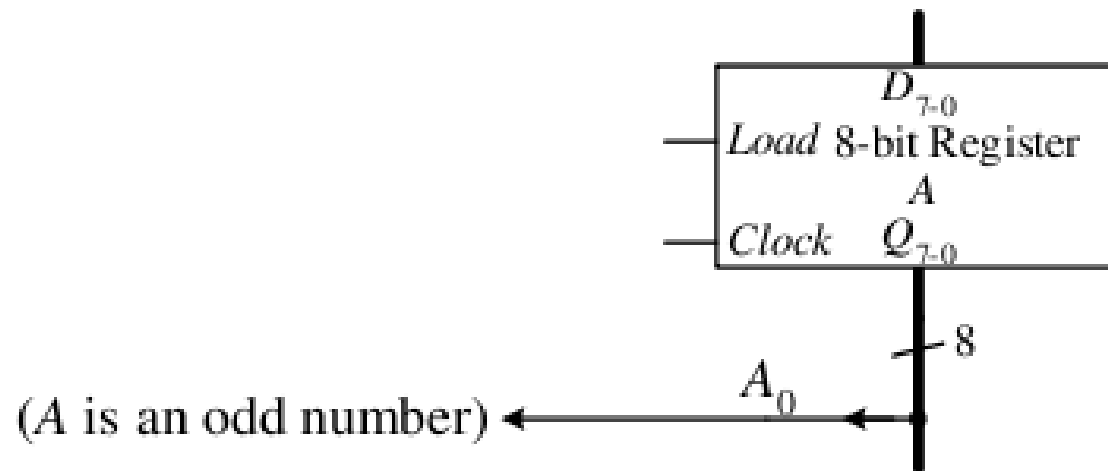

Examples of Dedicated Datapaths


- Simple if-then-else
- Counting 1 to 10
- Summation of n down to 1
- Factorial of n

Simple If-Then-Else

```

1      INPUT A
2      IF (A = 5) THEN
3          B = 8
4      ELSE
5          B = 13
6      END IF
7      OUTPUT B
    
```

Control Word	Instruction	ALoad	Muxsel	BLoad	Out
1	INPUT A	1	×	0	0
2	B = 8	0	1	1	0
3	B = 13	0	0	1	0
4	OUTPUT B	0	×	0	1

 


Counting 1 to 10


```

1      i = 0
2      WHILE (i ≠ 10) {
3          i = i + 1
4          OUTPUT i
5      }

```

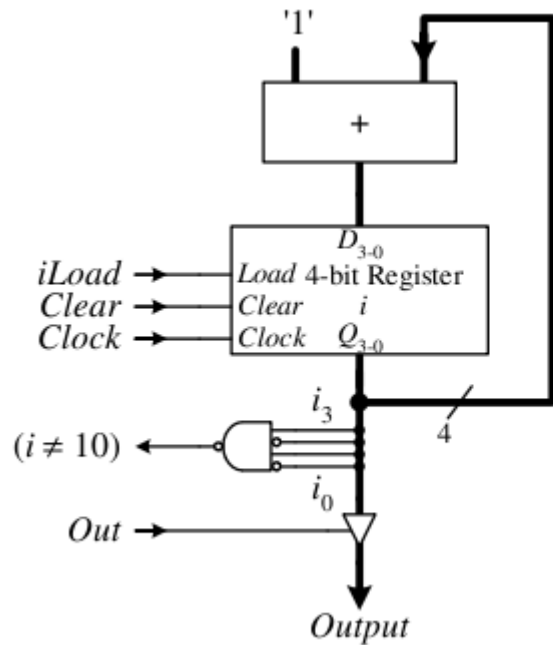

Control Word	Instruction	$iLoad$	$Clear$	Out
1	$i = 0$	0	1	0
2	$i = i + 1$	1	0	0
3	OUTPUT i	0	0	1

 


Control Word	Instruction	$Count$	$Clear$	Out
1	$i = 0$	0	1	0
2	$i = i + 1$	1	0	0
3	OUTPUT i	0	0	1

Summation of n Downto 1

```

 1      sum = 0
2      INPUT n
3      WHILE (n ≠ 0){
4          sum = sum + n
5          n = n - 1
6      }
7      OUTPUT sum
    
```




Control Word	Instruction	$nLoad$	$nCount$	$sumLoad$	$Clear$	Out
1	$sum = 0$	0	0	0	1	0
2	INPUT n	1	0	0	0	0
3	$sum = sum + n$	0	0	1	0	0
4	$n = n - 1$	0	1	0	0	0
5	OUTPUT sum	0	0	0	0	1

Factorial of n

```

1      INPUT  $n$ 
2       $product = 1$ 
3      WHILE ( $n > 1$ ) {
4           $product = product * n$ 
5           $n = n - 1$ 
6      }
7      OUTPUT  $product$ 

```

 

Control Word	Instruction	$productMux$	$productLoad$	$nLoad$	$nCount$	Out
1	INPUT n	×	0	1	0	0
2	$product = 1$	1	1	0	0	0
3	$product = product * n$	0	1	0	0	0
4	$n = n - 1$	×	0	0	1	0
5	OUTPUT $product$	×	0	0	0	1

Control Word	Instruction	$productMux$	$productLoad$	$nLoad$	$nCount$	Out
1	INPUT $n, product = 1$	1	1	1	0	0
2	$product = product * n, n = n - 1$	0	1	0	1	0
3	OUTPUT $product$	×	0	0	0	1

General Purpose Databath

```


1      sum = 0
2      INPUT n
3      WHILE (n ≠ 0){
4          sum = sum + n
5          n = n - 1
6      }
7      OUTPUT sum

```

ALU_2	ALU_1	ALU_0	Operation
0	0	0	Pass through A
0	0	1	A AND B
0	1	0	A OR B
0	1	1	NOT A
1	0	0	A + B
1	0	1	A - B
1	1	0	A + 1
1	1	1	A - 1

SH_1	SH_0	Operation
0	0	Pass through
0	1	Shift left and fill with 0
1	0	Shift right and fill with 0
1	1	Rotate right

Control Word	Instruction	IE 15	WE 14	$WA_{1,0}$ 13-12	RAE 11	$RAA_{1,0}$ 10-9	RBE 8	$RBA_{1,0}$ 7-6	$ALU_{2,1,0}$ 5-3	$SH_{1,0}$ 2-1	OE 0
1	sum = 0	0	1	00	1	00	1	00	101 (subtract)	00	0
2	INPUT n	1	1	01	0	xx	0	xx	xxx	xx	0
3	sum = sum + n	0	1	00	1	00	1	01	100 (add)	00	0
4	n = n - 1	0	1	01	1	01	0	xx	111 (decrement)	00	0
5	OUTPUT sum	x	0	xx	1	00	0	xx	000 (pass)	00	1

 

Example: Write the control words for manipulating the above circuit to perform the following program

Multiplication of two unsigned numbers:

```

1      prod = 0
2      INPUT A
3      INPUT B
4      WHILE (B ≠ 0) {
5          prod = prod + A
6          B = B - 1
7      }
8      OUTPUT prod
    
```

Control Word	Instruction	IE 15	WE 14	WA _{1,0} 13–12	RAE 11	RAA _{1,0} 10–9	RBE 8	RBA _{1,0} 7–6	ALU _{2,1,0} 5–3	SH _{1,0} 2–1	OE 0
1	<i>prod</i> = 0	0	1	00	1	00	1	00	101 (subtract)	00	0
2	INPUT A	1	1	01	0	xx	0	xx	xxx	xx	0
3	INPUT B	1	1	10	0	xx	0	xx	xxx	xx	0
4	<i>prod</i> = <i>prod</i> + A	0	1	00	1	00	1	01	100 (add)	00	0
5	<i>B</i> = <i>B</i> – 1	0	1	10	1	10	0	xx	111 (decrement)	00	0
6	OUTPUT <i>prod</i>	x	0	xx	1	00	0	xx	000 (pass)	00	1

VHDL for Datapath

16x8 RAM

```
entity ram_16_8 is port(
    cs:          in std_logic; -- chip select
    wr:          in std_logic; -- write / read enable
    addr:        in std_logic_vector(3 downto 0);
    di:          in std_logic_vector(7 downto 0); -- data in
    do:          out std_logic_vector(7 downto 0)); -- data out
end ram_16_8;

architecture imp of ram_16_8 is

    subtype cell is std_logic_vector(7 downto 0);
    type ram_type is array(0 to 15) of cell;
    signal RAM:      ram_type;

begin
    process(cs, wr)
        variable ctrl:      std_logic_vector(1 downto 0);

        begin
            ctrl := cs & wr;

            case ctrl is

                when "11" =>
                    RAM(conv_integer(addr)) <= di;
                    do <= di;
                when "10" =>
                    do <= RAM(conv_integer(addr));
                when others =>
                    do <= (others => 'Z');
            end case;

        end process;
    end imp;
```

256x8 ROM (Program Memory)

```
entity rom_256_8 is port(
    cs:          in std_logic;
    addr:        in std_logic_vector(7 downto 0);
    data:        out std_logic_vector(7 downto 0));
end rom_256_8;

architecture imp of rom_256_8 is

    subtype cell is std_logic_vector(7 downto 0);
    type rom_type is array(0 to 6) of cell;

    constant ROM:    rom_type :=(
inp & A,
dec & A,
outp & A,
jnz & "1011",
dec & A,
jnz & "1110",
nop);

begin

    process(cs)
    begin

        if(cs = '1') then
            data <= ROM(conv_integer(addr));
        else
            data <= (others => 'Z');
        end if;

    end process;

end imp;
```

2 bit Multiplexer

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;
use ieee.numeric_std.all;

entity mux2 is port(
    s:      in std_logic;
    x0, x1: in std_logic;
    y:      out std_logic);
end mux2;

architecture imp of mux2 is
begin
    process(s, x0, x1)
    begin
        if(s = '0') then
            y <= x0;
        else
            y <= x1;
        end if;
    end process;
end imp;
```

4 bit Multiplexer

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;
use ieee.numeric_std.all;

entity mux4 is port(
    S:      in std_logic_vector(1 downto 0);
    x0, x1, x2, x3: in std_logic;
    y:      out std_logic);
end mux4;

architecture imp of mux4 is
begin
    process(S, x0, x1, x2, x3)
    begin
        case S is
            when "00"    => y <= x0;
            when "01"    => y <= x1;
            when "10"    => y <= x2;
            when "11"    => y <= x3;
            when others  => y <= 'X';
        end case;
    end process;
end imp;
```

Register File

```
entity regfile is port(
  clk:          in std_logic;
  reset:        in std_logic;          -- reset
  we:           in std_logic;          -- write enable
  WA:           in std_logic_vector(1 downto 0); -- write address (4 registers)
  D:            in std_logic_vector(7 downto 0); -- input
  rbe:          in std_logic;
  RBA:          in std_logic_vector(1 downto 0); -- read address (4 registers)
  portA:        out std_logic_vector(7 downto 0);
  portB:        out std_logic_vector(7 downto 0));
end regfile;

architecture imp of regfile is

  subtype reg is std_logic_vector(7 downto 0);
  type regArray is array(0 to 3) of reg;
  signal RF: regArray;

begin
  WritePort: Process(clk, reset)
  begin
    if (clk'event and clk='1') then
      if (reset='1') then
        RF(0) <= (others => '0'); -- register A (accumulator)
        RF(1) <= (others => '0'); -- register B
        RF(2) <= (others => '0'); -- register F (Flag)
        RF(3) <= (others => '1'); -- register S (Stack Pointer)
      elsif (we='1') then
        RF(conv_integer(WA)) <= D;
      end if;
    end if;
  end process;

  ReadPortB: Process(rbe, RBA)
  begin
    if (rbe='1') then
      PortB <= RF(conv_integer(RBA));
    else
      PortB <= (others => 'X');
    end if;
  end process;

  ReadPortA: PortA <= RF(0); -- PortA always accumulator register
end imp;
```

Instruction Register


```
entity IR is port(  
    clk:          in std_logic;  
    reset:        in std_logic;          -- reset  
    load:         in std_logic;  
    INPUT :       in std_logic_vector(7 downto 0); -- input  
    OUTPUT:       out std_logic_vector(7 downto 0)); -- output  
end IR;  
  
architecture imp of IR is  
  
    subtype reg is std_logic_vector(7 downto 0);  
    signal IR8: reg;  
  
begin  
    Process(clk ,reset)  
    begin  
        if(clk'event and clk='1') then  
            if(reset='1') then  
  
                IR8 <= (others => '0');  
  
            elsif(load = '1') then  
  
                IR8 <= INPUT;  
  
            end if;  
  
            OUTPUT <= IR8;  
  
        end if;  
    end process;  
end imp;
```

Program Counter

```
entity PC is port(  
    clk:          in std_logic;  
    reset:        in std_logic;          -- reset  
    load:         in std_logic;  
    INPUT :      in std_logic_vector(7 downto 0); -- input  
    OUTPUT:      out std_logic_vector(7 downto 0)); -- output  
end PC;  
  
architecture imp of PC is  
  
    subtype reg is std_logic_vector(7 downto 0);  
  
    signal PC8: reg := "00000000";  
  
begin  
  
    Process(clk ,reset, load)  
    begin  
        if(clk'event and clk='1') then  
            if(reset='1') then  
  
                PC8 <= (others => '0');  
  
            elsif(load = '1') then  
  
                PC8 <= INPUT;  
  
            end if;  
        end if;  
    end process;  
  
    OUTPUT <= PC8;  
  
end imp;
```

Components of ALU


ALU and Shifter

 

s2	s1	s0	Function
0	0	0	Pass A to output
0	0	1	A and B
0	1	0	A or B
0	1	1	A'
1	0	0	A + B
1	0	1	A - B
1	1	0	A + 1
1	1	1	A - 1

s4	s3	Function
0	0	Pass through
0	1	Shift left and fill with 0
1	0	Shift right and fill with 0
1	1	Rotate right

 Adder/Subtractor with Arithmetic and Logic Extenders



Full Adder

```
entity FA is port(  
    carryIn:          in std_logic;  
    carryOut:         out std_logic;  
    x, y:             in std_logic;  
    s:                out std_logic);  
end FA;  
  
architecture imp of FA is  
begin  
    s <= x xor y xor carryIn;  
    carryOut <= (x and y) or (carryIn and (x xor y));  
end imp;
```

Arithmetic and Logic Extenders

s_2	s_1	s_0	Operation Name	Operation	x_i (LE)	y_i (AE)	c_0 (CE)
0	0	0	Pass	Pass A to output	a_i	0	0
0	0	1	AND	$A \text{ AND } B$	$a_i \text{ AND } b_i$	0	0
0	1	0	OR	$A \text{ OR } B$	$a_i \text{ OR } b_i$	0	0
0	1	1	NOT	A'	a_i'	0	0
1	0	0	Addition	$A + B$	a_i	b_i	0
1	0	1	Subtraction	$A - B$	a_i	b_i'	1
1	1	0	Increment	$A + 1$	a_i	0	1
1	1	1	Decrement	$A - 1$	a_i	1	0

(a)

s_2	s_1	s_0	x_i
0	0	0	a_i
0	0	1	$a_i b_i$
0	1	0	$a_i + b_i$
0	1	1	a_i'
1	$\times$	$\times$	a_i

s_2	s_1	s_0	b_i	y_i
0	$\times$	$\times$	$\times$	0
1	0	0	0	0
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	1

s_2	s_1	s_0	c_0
0	$\times$	$\times$	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

Logic Extender

```
entity LE is port(  
    S:                                in std_logic_vector(2 downto 0);  
    a, b:                             in std_logic;  
    x:                                out std_logic);  
end LE;  
  
architecture imp of LE is  
begin  
    process(S, a, b)  
    begin  
        case S is  
            when "000" => x <= a;  
            when "001" => x <= a and b;  
            when "010" => x <= a or b;  
            when "011" => x <= not a;  
            when others => x <= a;  
        end case;  
    end process;  
end imp;
```

Arithmetic Extender

```
entity AE is port(  
    S:                in std_logic_vector(2 downto 0);  
    a, b:             in std_logic;  
    y:                out std_logic);  
end AE;  
  
architecture imp of AE is  
begin  
    process(S, a, b)  
    begin  
        case S is  
            when "100" => y <= b;  
            when "101" => y <= not b;  
            when "110" => y <= '0';  
            when "111" => y <= '1';  
            when others => y <= '0';  
        end case;  
    end process;  
end imp;
```

8 bit LE

```
entity LE8 is port(  
    S:                                in std_logic_vector(2 downto 0);  
    A, B:                             in std_logic_vector(7 downto 0);  
    X:                                out std_logic_vector(7 downto 0));  
end LE8;  
  
architecture imp of LE8 is  
  
    component LE is port(  
        S:                                in std_logic_vector(2 downto 0);  
        a, b:                             in std_logic;  
        x:                                out std_logic);  
    end component;  
  
begin  
  
    U0: LE port map(S, A(0), B(0), X(0));  
    U1: LE port map(S, A(1), B(1), X(1));  
    U2: LE port map(S, A(2), B(2), X(2));  
    U3: LE port map(S, A(3), B(3), X(3));  
    U4: LE port map(S, A(4), B(4), X(4));  
    U5: LE port map(S, A(5), B(5), X(5));  
    U6: LE port map(S, A(6), B(6), X(6));  
    U7: LE port map(S, A(7), B(7), X(7));  
  
end imp;
```

8 bit AE

```
entity AE8 is port(  
    S:                                in std_logic_vector(2 downto 0);  
    A, B:                             in std_logic_vector(7 downto 0);  
    Y:                                out std_logic_vector(7 downto 0));  
end AE8;  
  
architecture imp of AE8 is  
  
    component AE is port(  
        S:                                in std_logic_vector(2 downto 0); --  
        a, b:                             in std_logic;  
        y:                                out std_logic);  
    end component;  
  
begin  
  
    U0: AE port map(S, A(0), B(0), Y(0));  
    U1: AE port map(S, A(1), B(1), Y(1));  
    U2: AE port map(S, A(2), B(2), Y(2));  
    U3: AE port map(S, A(3), B(3), Y(3));  
    U4: AE port map(S, A(4), B(4), Y(4));  
    U5: AE port map(S, A(5), B(5), Y(5));  
    U6: AE port map(S, A(6), B(6), Y(6));  
    U7: AE port map(S, A(7), B(7), Y(7));  
  
end imp;
```

addsub8

```
entity addsub8 is port(
    A:                in std_logic_vector(7 downto 0);
    B:                in std_logic_vector(7 downto 0);
    F:                out std_logic_vector(7 downto 0);
    carryIn:          in std_logic;
    unsigned_overflow: out std_logic;
    signed_overflow:   out std_logic);
end addsub8;

architecture imp of addsub8 is

    component FA port(
        carryIn:          in std_logic;
        carryOut:         out std_logic;
        x, y:             in std_logic;
        s:                out std_logic);
    end component;

    signal C:           std_logic_vector(7 downto 1);

begin
    U0: FA port map(carryIn, C(1), A(0), B(0), F(0));
    U1: FA port map(C(1), C(2), A(1), B(1), F(1));
    U2: FA port map(C(2), C(3), A(2), B(2), F(2));
    U3: FA port map(C(3), C(4), A(3), B(3), F(3));
    U4: FA port map(C(4), C(5), A(4), B(4), F(4));
    U5: FA port map(C(5), C(6), A(5), B(5), F(5));
    U6: FA port map(C(6), C(7), A(6), B(6), F(6));
    U7: FA port map(C(7), unsigned_overflow, A(7), B(7), F(7));

    signed_overflow <= C(7) xor C(6);
end imp;
```

Shifter

```
entity shifter8 is port(
    S:          in std_logic_vector(1 downto 0);
    A:          in std_logic_vector(7 downto 0);
    Y:          out std_logic_vector(7 downto 0);
    carryOut:   out std_logic;
    zero:       out std_logic);
end shifter8;

architecture imp of shifter8 is

    component mux4 is port(
        S:          in std_logic_vector(1 downto 0);
        x0, x1, x2, x3: in std_logic;
        y:          out std_logic);
    end component;

begin

    process(S) -- carry flag
    begin
        if(S="01") then
            carryOut <= A(7);
        elsif(S="10") then
            carryOut <= A(0);
        end if;
    end process;

    U0:    mux4 port map(S, A(0), '0', A(1), A(1), Y(0));
    U1:    mux4 port map(S, A(1), A(0), A(2), A(2), Y(1));
    U2:    mux4 port map(S, A(2), A(1), A(3), A(3), Y(2));
    U3:    mux4 port map(S, A(3), A(2), A(4), A(4), Y(3));
    U4:    mux4 port map(S, A(4), A(3), A(5), A(5), Y(4));
    U5:    mux4 port map(S, A(5), A(4), A(6), A(6), Y(5));
    U6:    mux4 port map(S, A(6), A(5), A(7), A(7), Y(6));
    U7:    mux4 port map(S, A(7), A(6), '0', A(0), Y(7));

    process(S) -- zero flag is set if the output of ALU is zero !! control the logic!
    begin
        if(S="00") then
            if(A=0) then
                zero <= '1';
            else
                zero <= '0';
            end if;
        end if;
    end process;

end imp;
```

ALU

```
entity ALU is port(
    S:                in std_logic_vector(4 downto 0);
    A, B:             in std_logic_vector(7 downto 0);
    F:                out std_logic_vector(7 downto 0);
    unsigned_overflow: out std_logic;
    signed_overflow:   out std_logic;
    carry:            out std_logic;
    zero:             out std_logic);
end ALU;

architecture imp of ALU is
    component LE8 is port(
        S:                in std_logic_vector(2 downto 0); -- Selection bits
        A, B:            in std_logic_vector(7 downto 0);
        X:                out std_logic_vector(7 downto 0));
    end component;

    component AE8 is port(
        S:                in std_logic_vector(2 downto 0); -- Selection bits
        A, B:            in std_logic_vector(7 downto 0);
        Y:                out std_logic_vector(7 downto 0));
    end component;

    component addsub8 is port(
        A:                in std_logic_vector(7 downto 0);
        B:                in std_logic_vector(7 downto 0);
        F:                out std_logic_vector(7 downto 0);
        carryIn:          in std_logic;
        unsigned_overflow: out std_logic;
        signed_overflow:   out std_logic);
    end component;

    component shifter8 is port(
        S:                in std_logic_vector(1 downto 0);
        A:                in std_logic_vector(7 downto 0);
        Y:                out std_logic_vector(7 downto 0);
        carryOut:         out std_logic;
        zero:             out std_logic);
    end component;

    signal X, Y, ShiftInput: std_logic_vector(7 downto 0);
    signal c0:               std_logic;

begin
    CarryExtender_ALU: c0 <= (S(0) xor S(1)) and S(2);
    LogicExtender8_ALU: LE8 port map(S(2 downto 0), A, B, X);
    ArithmeticExtender8_ALU: AE8 port map(S(2 downto 0), A, B, Y);
    AddSub8_ALU: addsub8 port map(X, Y, ShiftInput, c0, unsigned_overflow, signed_overflow);
    Shifter8_ALU: shifter8 port map(S(4 downto 3), ShiftInput, F, carry, zero);
end imp;
```